

VLSI
PROGRAMMABLE BINARY TREE COMPUTATION
CHIP NAME: PBTCKS

Samir Silbak¹ and Manasa Kasula²

¹silbaksr@mail.uc.edu

²kasulama@mail.uc.edu

¹(513) 207-0687

²(847) 612-7364

November 12, 2013

Contents

1	Pinout Diagram	6
1.1	Pinout Description	7
2	Explanation of Chip Function	8
2.1	Configuration of Chip	8
3	Inclusion and Explanation of the Test Mode	9
4	Major Design Decisions	9
5	Block Diagrams	10
5.1	Top Level Diagram	10
5.2	Top Level Diagram: LUT Slice and Shift Slice	10
5.3	Bit Slice Design Scheme	11
5.4	Top Level Test Mode Diagram	12
6	VHDL Models with Test Mode	13
6.1	Top Level Module	13
6.2	Slice Modules	15
6.2.1	LUT	15
6.2.2	Shift Register	16
6.3	Gates	17
6.3.1	D-Flip Flop	17
6.3.2	2:1 Multiplexer	17
6.4	VHDL Test Benches	18
7	VHDL Waveform Plots and Results	21
8	Work Division	24
9	Magic Layouts	25
9.1	LUT Slice Layout	25
9.2	Shift Slice Layout	25
10	IRSIM Simulations	26
10.1	Bit Slice Simulations	26
11	Gate Level Simulations	28
12	HSpice Simulations	29
12.1	Bit Slice Simulations	29
12.2	Gate Level Simulations	31
13	VHDL Modules with Delay	33
13.1	VHDL Test Bench Modules with Delay	37
13.2	VHDL Gate Modules with Delay	40
14	VHDL Modules Delay Waveforms	41
15	Floor Plan	44

16 Major Design Decisions	45
17 Work Division	45
18 Chip Level Layout	46
19 Users Guide	46
20 Test Strategy	47
21 Description of Chip Architecture	48
22 Major Design Decisions	48
23 IRSIM Simulations	50
24 VHDL Simulations	52
25 Simulation Strategy	52
26 Work Division	53

List of Figures

1	Pinout Diagram of the PBTCKS Chip	6
2	Cycle Timing Diagram for LUT Shift Register	8
3	Cycle Timing Diagram for P Input Shift Register	8
4	First Top Level Diagram (8 Inputs, 28-bit slice)	10
5	Top Level Diagram (8 Inputs, 28-bit slice)	10
6	New Designed Top Level Diagram (8 Inputs, 28-bit slice)	11
7	LUT Slice in Logisim	11
8	Top Level Test Mode Diagram (8 Inputs, 28-bit slice)	12
9	New Designed Top Level Test Mode Diagram (8 Inputs, 28-bit slice)	12
10	RTL Design of Top Level	14
11	RTL Design of LUT Slice	16
12	RTL Design of Shift Register Slice	17
13	AND Gate of LUT Slice	21
14	NAND Gate of LUT Slice	22
15	OR Gate of LUT Slice	22
16	NOR Gate of LUT Slice	22
17	XOR Gate of LUT Slice	23
18	Waveform for Top Test Bench	23
19	Waveform for Top Test Bench for Test Enabled	23
20	LUT Slice Magic Layout	25
21	LUT Slice Internal Magic Layout	25
22	Shift Slice Magic Layout	25
23	Shift Slice Internal Magic Layout	26
24	LUT Slice with AND gate 'programmed'	26
25	Rising Edge of F output of LUT Slice	26
26	Falling Edge of F output of LUT Slice	27
27	Rising Edge of L3 DFF of LUT Slice	27
28	Falling Edge of L3 DFF of LUT Slice	27
29	Rising Edge of DFF of Shift Slice	27
30	Falling Edge of DFF of Shift Slice	27
31	Waveform of DFF of Shift Slice	28
32	Rising Edge of Inverter	28
33	Falling Edge of Inverter	28
34	Waveform of LUT Slice (Includes nodes at each flip flop)	28
35	Hspice LUT Slice Waveform	29
36	Hspice Delay of Shift Register Slice	30
37	Hspice Shift Register Slice Waveform	30
38	Hspice Delay of DFF	31
39	Hspice Delay of Inveter	31
40	Hspice Delay of Mux	32
41	Delay Waveform of DFF	41
42	Delay Waveform of MUX	42
43	Delay Waveform of Inverter	42
44	Top Level Delay Waveform	42
45	Top Level Delay Waveform Zoomed In	43
46	Top Level Test Mode Enabled Delay Waveform	43
47	Top Level Test Mode Enabled Delay Waveform Zoomed In	43
48	32 Bit Floor Plan Design	44

49	64 Bit Floor Plan Design	45
50	32 Bit Layout - Magic	46
51	Cycle Timing Diagram for Normal Mode	46
52	Cycle Timing Diagram for Test Mode Enable	47
53	64 Bit Layout in Magic	49
54	Top Delay Normal Mode	50
55	Test LUT Slice	50
56	Test P Shift Register Slice	51
57	Test DFF Slice	51
58	Inverter	51
59	Top 32-bit Normal Mode	52
60	Top 32-bit Test Mode	52
61	Top Delay 32-bit Normal Mode	52
62	Top Delay 32-bit Test Mode	52
63	Debug Mode in IRSIM	53

List of Tables

1	Pinout Description	7
2	AND Gate Truth Table	8
3	Task Assignment	24
4	Leaf Level Component Delay Times	32
5	Bit Slice Worst Case Delay Times	43
6	Task Assignment	45
7	Capacitance Values for D-Flip-Flop	49
8	Capacitance Value and Output Drive Strength for Buffer	49
9	Total Delay Times for Normal Mode between VHDL and IRSIM	52
10	Task Assignment	53

Listings

1	Top Module	13
2	Lookup Table Slice Module	15
3	Lookup Table Slice Module	16
4	D-Flip Flop Module	17
5	2:1 Multiplexer Module	18
6	LUT Slice Test Bench Module	18
7	Top Level Test Bench Module	19
8	Top Module Delay	33
9	Look Up Table Module Delay	33
10	Look Up Table Slice Module Delay	35
11	Test Mode Enabled Test Bench	37
12	Top Module Test Bench	38
13	DFF Module Delay	40
14	Inverter Module Delay	40
15	Inverter Module Delay	41

1 Pinout Diagram

 


Figure 1: Pinout Diagram of the PBTCKS Chip

1.1 Pinout Description

Function	Pin #	I/O	Description
–	1	–	–
–	2	–	–
LO4	3	–	Last 16 Array Bit LUT Ouput
PCLKI	4	I	P Shift Register Clock Input
LCLKI	5	I	LUT Shift Register Clock Input
PIN	6	I	P Shift Register Input
LIN	7	I	LUT Shift Register Input
TMEI	8	I	Test Mode Enabled Input
–	9	–	–
–	10	–	–
TII	11	I	Test Inverter Input
TIO	12	O	Test Inverter Output
TFDI	13	I	Test Flip-Flop D Input
TFCI	14	I	Test Flip-Flop Clock Input
TFCO	15	O	Test Flip-Flop Clock Output
GND	16	–	Ground Reference for I/O Pins
TFQO	17	O	Test Flip-Flop Q Output
PO1	18	–	First 8 Bit P Array Output
LO1	19	–	First 16 Bit LUT Array Output
–	20	–	–
–	21	–	–
–	22	–	–
TMEO	23	O	Test Mode Enabled Output
LOUT	24	O	P Shift Register Output of P input
POUT	25	O	P Shift Register Output of LUT
PCLKO	26	O	LUT Shift Register Clock Output
PCLKO	27	O	P Shift Register Clock Output
F	28	O	Output of Computation of LUT
–	29	–	–
–	30	–	–
TPO	31	O	Test P Slice Output
TPI	32	I	Test P Slice Input
TSF	33	O	Test LUT Slice Mux Output
TSLO	34	O	Test LUT Slice Shift Register Output
TSB	35	I	Test LUT Slice B Address Input
VDD	36	I	Test LUT Slice B Input
TSA	37	I	Test LUT Slice A Address Input
TSLI	38	I	Test LUT Slice Shift Register Input
TSCO	39	O	Test LUT Slice Clock Output
TSCI	40	I	Test LUT and P SLice Clock Input

Table 1: Pinout Description

2 Explanation of Chip Function

The main functionality of the chip is to be able to take N-bit inputs and compute the combinational logic among all N-bit inputs. Each node in the binary tree is what constitutes the combinational function of two inputs. Each node is described to be a 4-bit Look Up Table (LUT). The LUT has the function of any combinational function the user wants to perform. For example, for an AND gate, the user must shift in “0001” into the LUT. Each LUT of all the nodes together create the “program” which are all cascaded together to perform a shift register. The binary tree accepts the input P and produces only a single bit output F. For example, if the user has 8 different inputs, an example of the function can be described as so: (A or B) or (C or D) or (E or F) or (G or H). Here we can see that we have 8 different inputs performing 7 different functions (in this case each function is the same) and only one single output, F. P is defined to be twice the number of leaf nodes in the binary tree, and the input is shifted in serially using a shift register. In order to “program” the LUTs with the specific functions, these also must be shifted in serially using a shift register. Therefore, going back to the case where we have 8 different inputs and 7 different LUTs, we can see that we will have to shift in 28 (7×4) bits into the LUT shift register. Each set of LUT outputs are connected to a 2:1 multiplexer to choose the output of the function. What this means is that the inputs can be thought of the address line into the LUT—what ever value happens to be stored is the result of that computation. For example, the figure below shows the truth table for an AND gate, we see inputs A and B, these are the address lines into the LUT. Therefore, we see that the output value of the LUT can only be 1 in the last row of the truth table, this method is very efficient and in fact this is how FPGAs/ASICs work, they use LUTs to perform these combinational functions.

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

Table 2: AND Gate Truth Table

2.1 Configuration of Chip

 


Figure 2: Cycle Timing Diagram for LUT Shift Register

Here we can see that the only thing the user needs to do is shift in the “function” wanted among the inputs. Since the data bits get loaded in from MSB to LSB, the user must input the function in reversed order. For example, if we want to perform an AND operation, we have to feed the data bits in like so: 1000.

 


Figure 3: Cycle Timing Diagram for P Input Shift Register

As described from above the user has to just feed in input P, but in reversed order. Note that in test mode, the user has to just toggle the TMEI high.

3 Inclusion and Explanation of the Test Mode

In order to enable the test mode, the user must set the TMEI pin high. In doing so, we will bypass the last output of P and feed it into the shift register input of the LUT. This will connect all the flip flops together, and we can perform our scan chain to make sure the inputs are being shifted the way they are supposed to be. We will be able to monitor the output on the TMEO pin. Since only one clock line is required, we bypass the LUT clock line by just hooking up the clock line of the P shift register. If test mode is disabled however, then the circuit will perform back to its original function.

4 Major Design Decisions

The first thing that needed to be accomplished was to assemble the bit-slice design with minimal hardware and hardware that was supported by the library given to us. For example, our LUT bit slice uses three 2:1 Multiplexers, we could have used a 4:1 multiplexer, but having done so, our design would have been more complex when designing our Magic layouts.

We also wanted to make sure that the wiring would not be too complex between each LUT slice. Since this is a binary tree computation, we made sure to hook up the hardware in that fashion as it made it much easier to visualize how this needed to be connected while keeping in mind that we must connect each one to achieve the desirable 50MHz clock frequency.

5 Block Diagrams

5.1 Top Level Diagram

 


Figure 4: First Top Level Diagram (8 Inputs, 28-bit slice)

5.2 Top Level Diagram: LUT Slice and Shift Slice

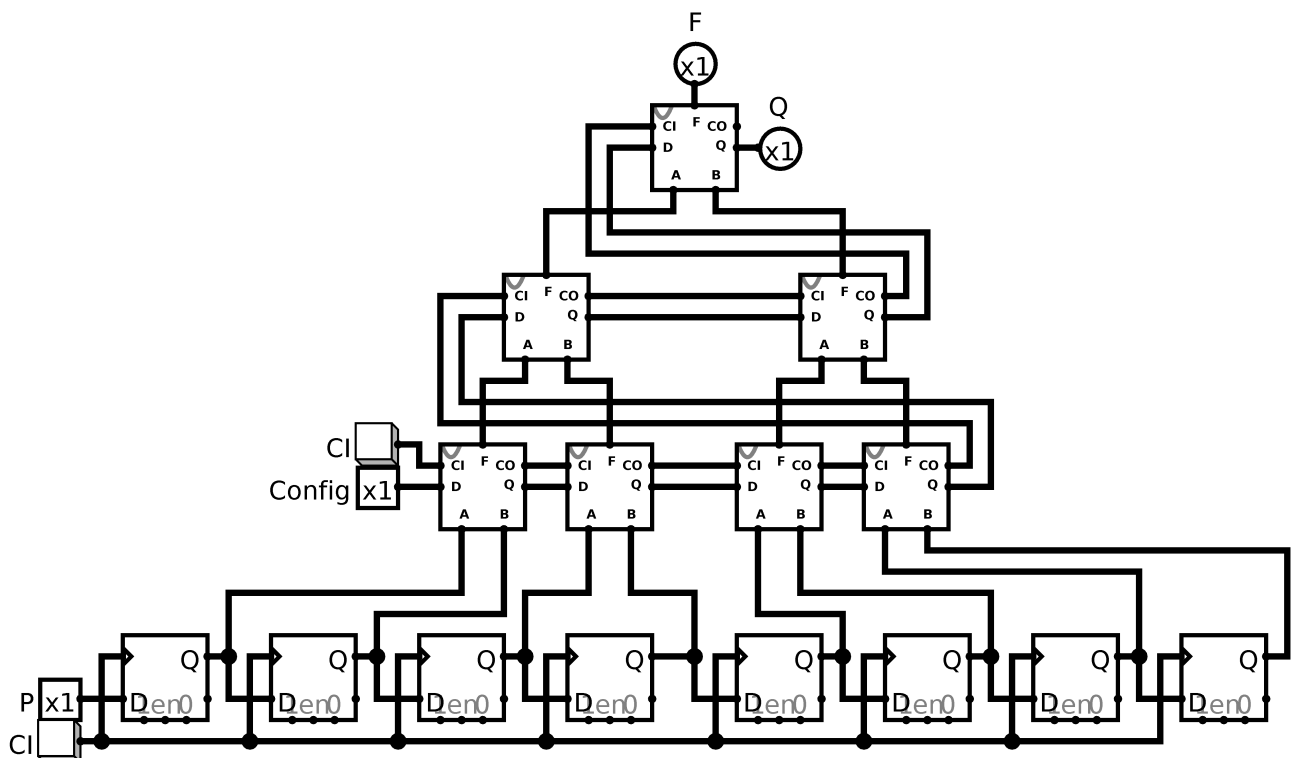


Figure 5: Top Level Diagram (8 Inputs, 28-bit slice)

We can see that the slice design of the P shift register is just made up of D-flip flops as shown in the above top level diagram for input P. Here we can see that we have P being twice the leaf nodes (8 in this case) and the LUTs are all cascaded together giving us a total width vector of 28 bits.

 


Figure 6: New Designed Top Level Diagram (8 Inputs, 28-bit slice)

We came up with a new design of how we will lay the chip out. This new design (more explained in major design decisions) takes full advantage of the total area given to us.

5.3 Bit Slice Design Scheme

 


Figure 7: LUT Slice in Logisim

Here we can see we have three 2:1 multiplexers, and 4 D-flip flops. We have the input of the LUT getting shifted through the d-flip flops. Each set of two outputs from the D-flip flops are connected to the inputs of the mux on select line A. Then the output from each mux will be fed into the final mux performing the computation on select line B.

5.4 Top Level Test Mode Diagram

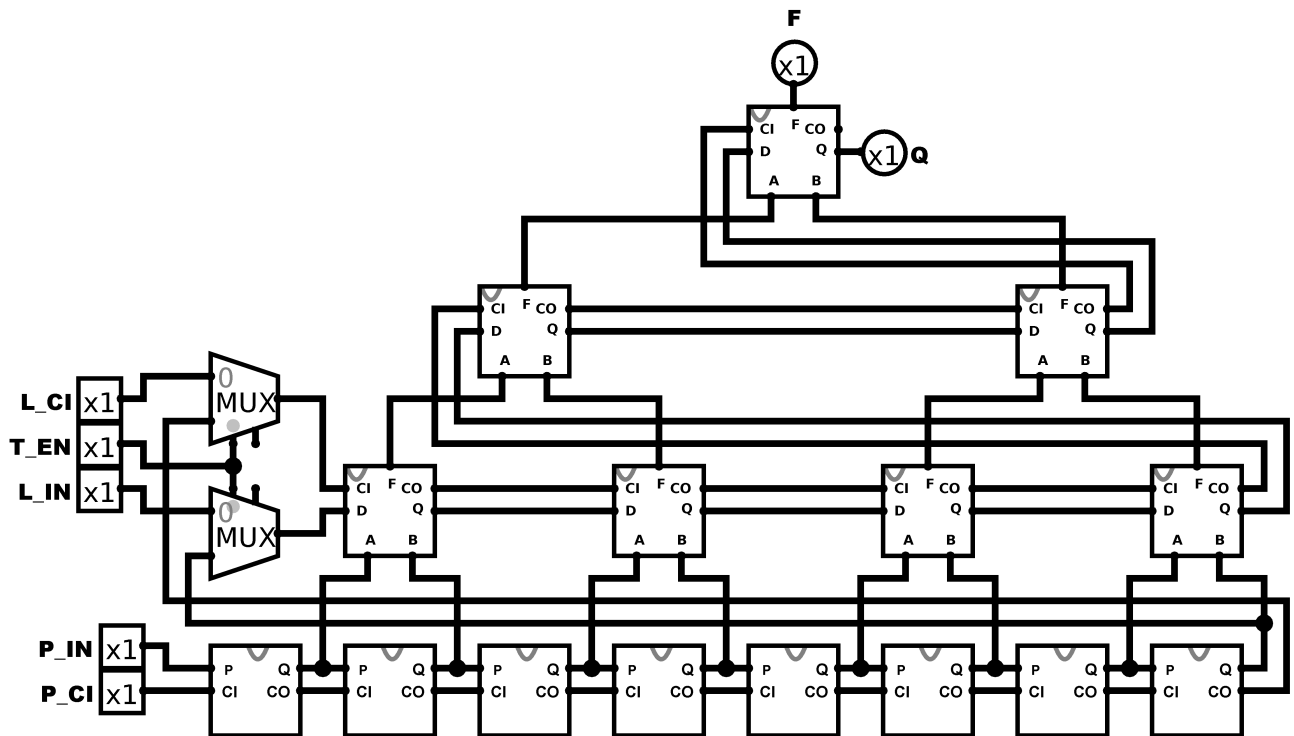


Figure 8: Top Level Test Mode Diagram (8 Inputs, 28-bit slice)

 


Figure 9: New Designed Top Level Test Mode Diagram (8 Inputs, 28-bit slice)

This test mode is configured with two 2:1 multiplexers. Each multiplexer will select the input line whether we are in test or normal mode. In test mode enabled, we see that we need to feed in the last output of the shift register into the input of L_IN, where L_IN is the input data into the LUT. Also, the clock used to shift the P data in, must now be the same clock input for the LUT. If test mode is disabled, we can see that the multiplexer will select the L_IN to be the data configured by the user (not the data outputted from P).

6 VHDL Models with Test Mode

6.1 Top Level Module

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity top is
5      generic(
6          n      : integer := 2    -- number of levels in tree
7      );
8      port(
9          p_clk : in std_logic;    -- shift register clock
10         l_clk : in std_logic;    -- lut shift register clock
11         p_in  : in std_logic;    -- shift register input (P)
12         l_in  : in std_logic;    -- lut shift register input
13         t_en  : in std_logic;    -- test enable input
14         f_o   : out std_logic;   -- final output of computation
15         q_o   : out std_logic;   -- final lut shift register output
16     );
17 end top;
18
19 architecture rtl of top is
20
21     signal shift_clki : std_logic := '0';
22     signal shift_clk  : std_logic := '0';
23     signal l_shf_ini  : std_logic := '0';
24     signal l_shf_in   : std_logic := '0';
25     signal p_out      : std_logic := '0';
26
27 begin
28
29     -- test mux connects output of P into input of LUT and use same clock line
30     t_mux_1 : entity work.mux2x1 port map(l_clk , p_clk , t_en , shift_clki);
31     t_mux_2 : entity work.mux2x1 port map(l_in , p_out , t_en , l_shf_ini);
32
33     t_inv_1 : entity work.invx1 port map(shift_clki , shift_clk);
34     t_inv_2 : entity work.invx1 port map(l_shf_ini , l_shf_in);
35
36     lut_1 : entity work.lut
37     generic map(
38         n      => n
39     )
40     port map(
41         s_clk => p_clk ,
42         l_clk => shift_clk ,
43         s_in  => p_in ,
44         l_in  => l_shf_in ,
45         t_po  => p_out ,
46         f_o   => f_o ,
47         q_o   => q_o
48     );
49
50 end rtl;

```

Listing 1: Top Module

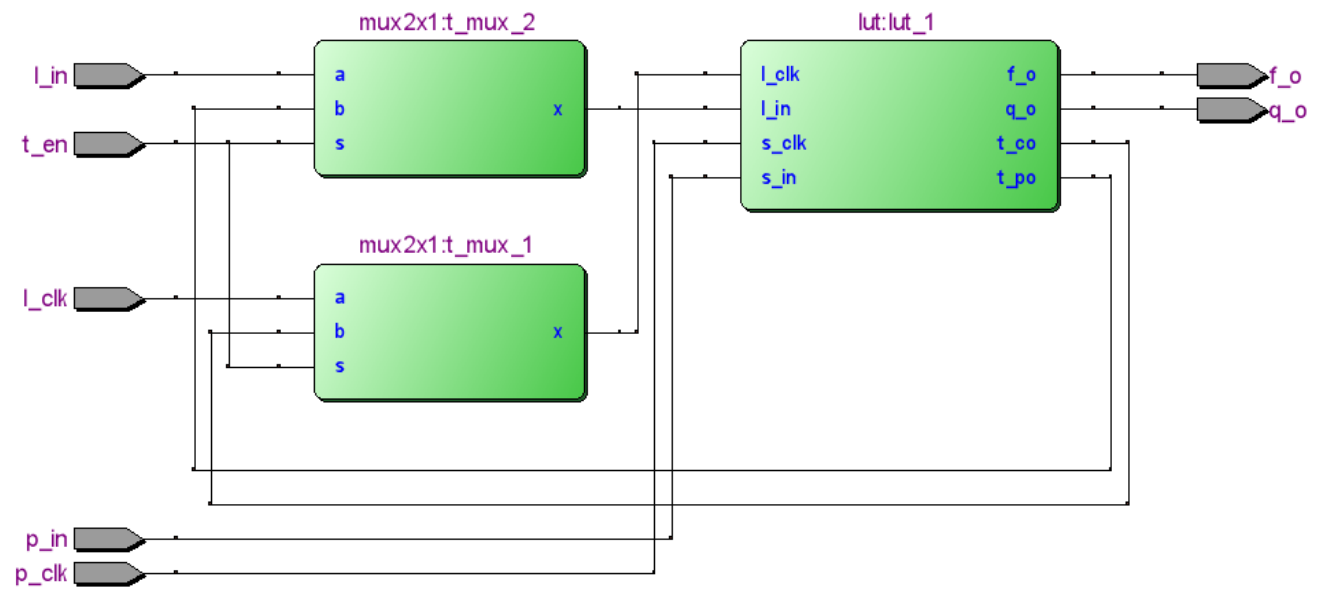


Figure 10: RTL Design of Top Level

6.2 Slice Modules

6.2.1 LUT

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity lut_slice is
6      port(
7          clk_i    : in std_logic;
8          d        : in std_logic;
9          a        : in std_logic;
10         b        : in std_logic;
11         q        : out std_logic;
12         f        : out std_logic
13     );
14 end lut_slice;
15
16 architecture rtl of lut_slice is
17
18     component dffposx1 is
19         port(
20             clk : in std_logic;
21             d   : in std_logic;
22             q   : out std_logic
23         );
24     end component;
25
26     component mux2x1 is
27         port(
28             b : in std_logic;
29             a : in std_logic;
30             s : in std_logic;
31             x : out std_logic
32         );
33     end component;
34
35     component invx1 is
36         port(
37             a : in std_logic;
38             x : out std_logic
39         );
40     end component;
41
42     — flip flop and mux outputs
43     signal ff_o      : std_logic_vector(4 downto 0) := (others => '0');
44     signal mux_o     : std_logic_vector(1 downto 0) := (others => '0');
45     signal mux_fo    : std_logic_vector(1 downto 0) := (others => '0');
46     signal f_muxo    : std_logic := '0';
47
48     begin
49
50     — shifting in from LSB to MSB
51     shift_gen_lut : for i in 0 to 3 generate
52         ff_lut_i : dffposx1
53         port map(
54             clk => clk_i ,
55             d   => ff_o(i),
56             q   => ff_o(i+1)
57         );
58     end generate;
59

```

```

60  -- lut shift out is output from prev ff
61  q <= ff_o(4);
62  ff_o(0) <= d;
63
64  -- select first two outputs of LUT
65  -- on sel line A
66  mux1 : mux2x1 port map(ff_o(1), ff_o(2), a, mux_o(0));
67  inv1 : invx1 port map(mux_o(0), mux_fo(0));
68
69  -- select last two outputs of LUT
70  -- on sel line A
71  mux2 : mux2x1 port map(ff_o(3), ff_o(4), a, mux_o(1));
72  inv2 : invx1 port map(mux_o(1), mux_fo(1));
73
74  -- select the outputs from
75  -- each mux on sel line B
76  mux3 : mux2x1 port map(mux_fo(0), mux_fo(1), b, f_muxo);
77
78  -- invert mux due to func of mux: y=!(S?(A:B))
79  inv3 : invx1 port map(f_muxo, f);
80
81  end rtl;

```

Listing 2: Lookup Table Slice Module

 


Figure 11: RTL Design of LUT Slice

6.2.2 Shift Register

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity shift_slice is
5      port(
6          clk_i    : in std_logic;
7          p        : in std_logic;
8          clk_o    : out std_logic;
9          q        : out std_logic
10     );
11  end shift_slice;
12
13  architecture rtl of shift_slice is
14
15      component dffposx1
16          port(
17              clk : in std_logic;
18              d   : in std_logic;
19              q   : out std_logic
20          );
21      end component;
22
23  begin

```



```

24
25     ff_p1 : dffposx1
26     port map(
27         clk => clk_i ,
28         d   => p,
29         q   => q
30     );
31
32     clk_o <= clk_i;
33
34 end rtl;

```

Listing 3: Lookup Table Slice Module

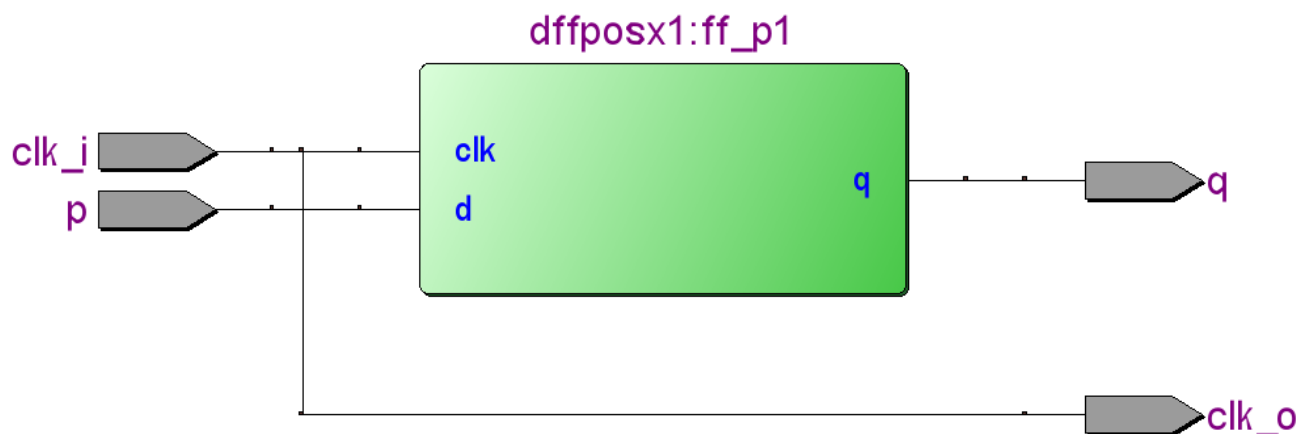


Figure 12: RTL Design of Shift Register Slice

6.3 Gates

6.3.1 D-Flip Flop

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity dffposx1 is
5      generic(
6          delay : time := 0 ps
7      );
8      port(
9          clk : in std_logic;
10         d   : in std_logic;
11         q   : out std_logic
12     );
13 end dffposx1;
14
15 architecture rtl of dffposx1 is begin
16     process(clk) begin
17         if rising_edge(clk) then
18             q <= d after delay;
19         end if;
20     end process;
21 end rtl;

```

Listing 4: D-Flip Flop Module

6.3.2 2:1 Multiplexer

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity mux2x1 is
5      generic(
6          delay : time := 0 ps
7      );
8      port(
9          b : in std_logic;
10         a : in std_logic;
11         s : in std_logic;
12         x : out std_logic
13     );
14 end mux2x1;
15
16 architecture rtl of mux2x1 is begin
17
18     x <= not(b) after delay when (s = '0') else
19         not(a) after delay when (s = '1');
20
21 end rtl;

```

Listing 5: 2:1 Multiplexer Module

6.4 VHDL Test Benches

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity lut_slice_tb is
6  end lut_slice_tb;
7
8  architecture behavior of lut_slice_tb is
9
10     signal clk      : std_logic := '0';
11     signal di       : std_logic := '0';
12     signal a        : std_logic := '0';
13     signal b        : std_logic := '0';
14     signal q        : std_logic;
15     signal f        : std_logic;
16
17     component lut_slice
18     port(
19         clk_i      : in std_logic;
20         d          : in std_logic;
21         a          : in std_logic;
22         b          : in std_logic;
23         q          : out std_logic;
24         f          : out std_logic
25     );
26 end component;
27
28 begin
29
30     dut : lut_slice
31     port map(
32         clk_i  => clk,
33         d      => di,
34         a      => a,
35         b      => b,
36         q      => q,

```

```

37         f      => f
38     );
39
40     process
41
42         procedure clock is begin
43             clk <= '1';
44             wait for 10 ns;
45             clk <= '0';
46             wait for 10 ns;
47         end procedure clock;
48
49     begin
50
51         wait for 10 ns;
52         a  <= '1';
53         b  <= '1';
54
55         -- lut for AND gate
56         di <= '1';
57         wait for 10 ns;
58         clock;
59
60         di <= '0';
61         wait for 10 ns;
62         clock;
63
64         di <= '0';
65         wait for 10 ns;
66         clock;
67
68         di <= '0';
69         wait for 10 ns;
70         clock;
71
72         wait;
73
74     end process;
75
76 end behavior;

```

Listing 6: LUT Slice Test Bench Module

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use std.textio.all;
4  use work.txt_util.all;
5
6  entity top_tb is
7      generic(
8          --stim_file : string := "test_tree.sim"
9          --stim_file : string := "two_tree.sim"
10         stim_file : string := "top_32.sim"
11     );
12 end top_tb;
13
14 architecture behavior of top_tb is
15
16     constant n : integer := 5;
17
18     signal p_clk : std_logic := '0';
19     signal l_clk : std_logic := '0';
20     signal p      : std_logic := '0';

```

```

21  signal l_in  : std_logic := '0';
22  signal f_o   : std_logic;
23  signal q_o   : std_logic;
24  signal t_en  : std_logic := '0';
25
26  signal p_in_vector : std_logic_vector((2**n)-1 downto 0);
27  signal lut_vector  : std_logic_vector((((2**n)-1)*4)-1 downto 0);
28
29  file stimulus : TEXT open read_mode is stim_file;
30
31  component top
32    generic(
33      n      : integer := 3      -- number of levels in tree
34    );
35    port(
36      p_clk : in std_logic;      -- p shift register clock
37      l_clk : in std_logic;      -- lut shift register clock
38      p_in  : in std_logic;      -- shift register input (P)
39      l_in  : in std_logic;      -- lut shift register input
40      t_en  : in std_logic;      -- test enable input
41      f_o   : out std_logic;     -- final output of computation
42      q_o   : out std_logic      -- lut shift register output
43    );
44  end component;
45
46  begin
47
48    dut : top
49      generic map(
50        n      => n
51      )
52      port map(
53        p_clk => p_clk ,
54        l_clk => l_clk ,
55        p_in  => p ,
56        l_in  => l_in ,
57        t_en  => t_en ,
58        f_o   => f_o ,
59        q_o   => q_o
60      );
61
62    process
63
64      procedure clk_p_in is begin
65        p_clk <= '1';
66        wait for 10 ns;
67        p_clk <= '0';
68        wait for 10 ns;
69      end procedure clk_p_in;
70
71      procedure clk_lut_in is begin
72        l_clk <= '1';
73        wait for 10 ns;
74        l_clk <= '0';
75        wait for 10 ns;
76      end procedure clk_lut_in;
77
78      variable l: line;
79      variable p_in_str : string(1 to 2**n);
80      variable l_shf_str: string(1 to ((2**n)-1)*4);
81
82    begin
83
84      while not endfile(stimulus) loop

```

```

85
86      — load stimulus for this test
87      readline(stimulus, l); read(l, p_in_str);
88      p_in_vector <= to_std_logic_vector(p_in_str);
89
90      readline(stimulus, l); read(l, l_shf_str);
91      lut_vector <= to_std_logic_vector(l_shf_str);
92
93      wait for 50 ns;
94
95      — clock in the P input
96      for i in 0 to (2**n)-1 loop
97          p <= p_in_vector(i);
98          wait for 10 ns;
99          clk_p_in;
100      end loop;
101
102      — clock in the "program" (lut functions)
103      for i in 0 to (((2**n)-1)*4)-1 loop
104          l_in <= lut_vector(i);
105          wait for 10 ns;
106          clk_lut_in;
107      end loop;
108
109  end loop;
110
111  report "Test Complete" severity note;
112  wait;
113
114  end process;
115
116  end behavior;

```

Listing 7: Top Level Test Bench Module

7 VHDL Waveform Plots and Results

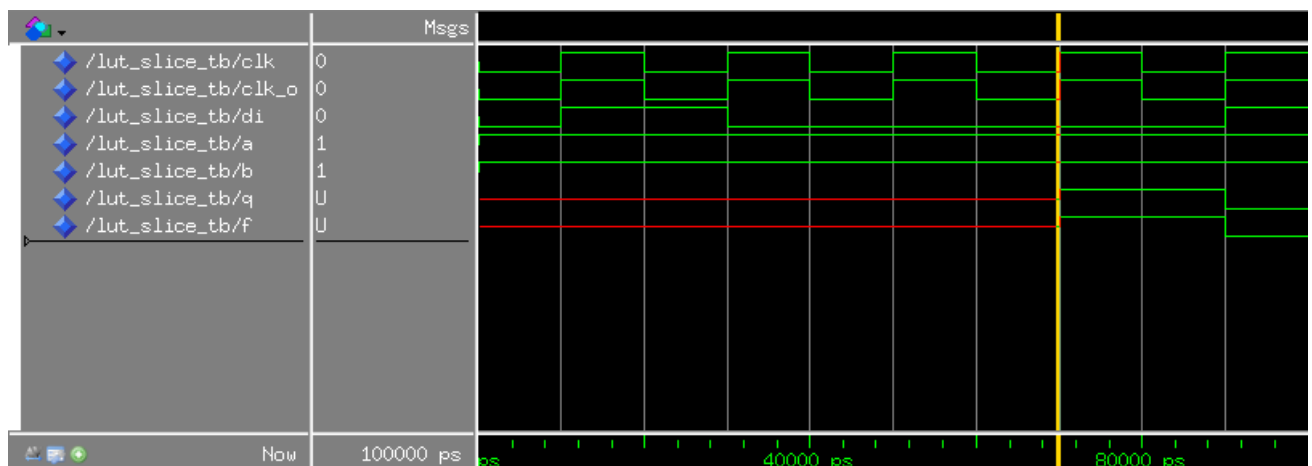


Figure 13: AND Gate of LUT Slice

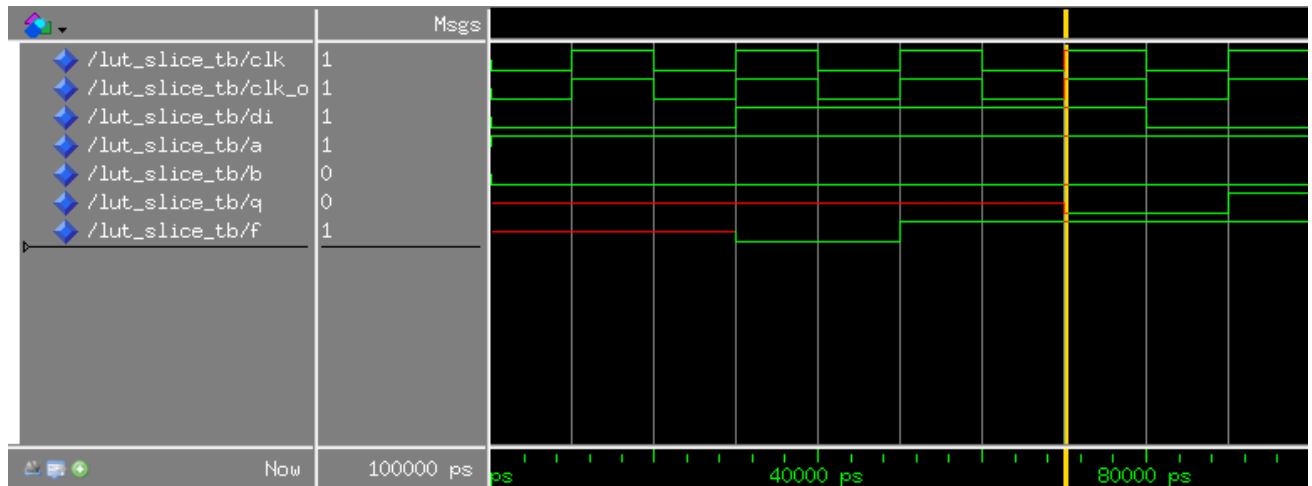


Figure 14: NAND Gate of LUT Slice

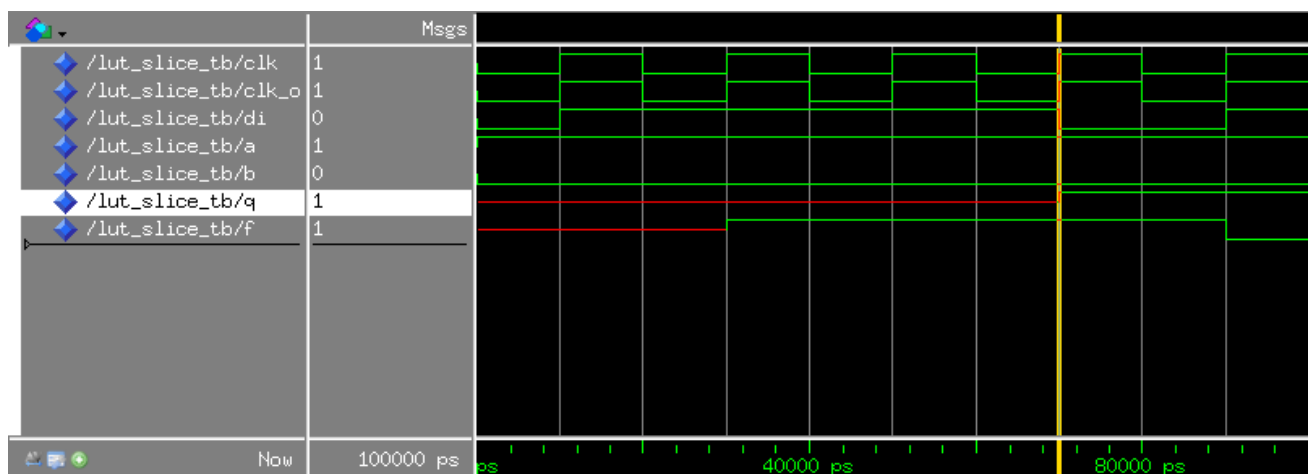


Figure 15: OR Gate of LUT Slice

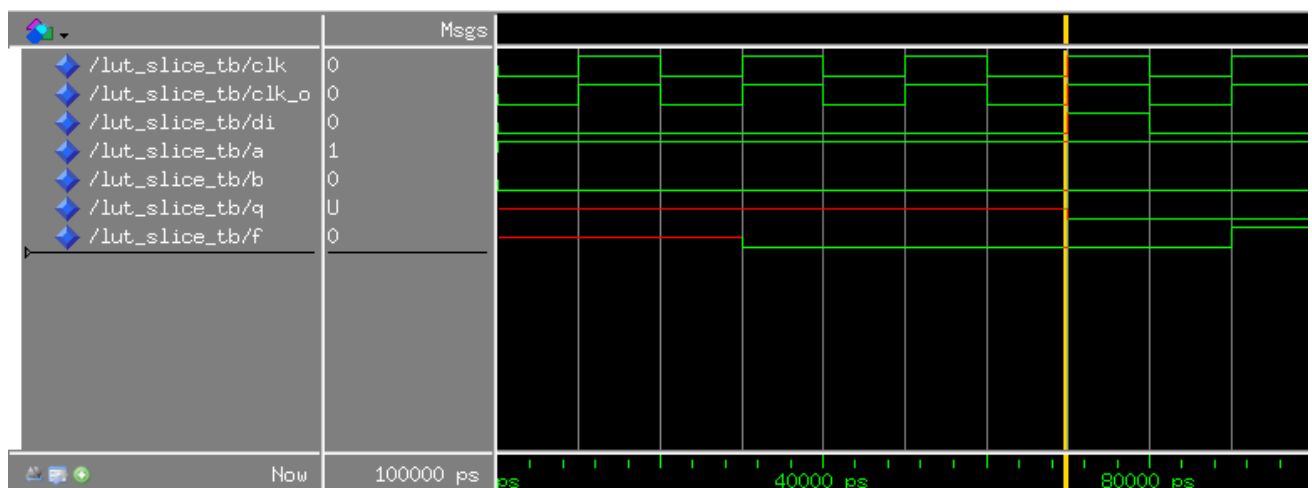


Figure 16: NOR Gate of LUT Slice

 


Figure 17: XOR Gate of LUT Slice

Before we could go on with designing the top level in VHDL, we had to make sure that the slice itself worked first. Here we are just showing just a few waveforms from each function. As we can see here, each gate that was tested performed as expected.



Figure 18: Waveform for Top Test Bench

Since we are testing with 8 input values, there are $2^{(28/4)}$ combinations for the combinational functions. Since that is way more than we can test, we selected a few to test. We can see the results in the above waveform (Test Mode Disabled).

 


Figure 19: Waveform for Top Test Bench for Test Enabled

This is with Test Enabled for $N=2$. Here we can see the output of F at the very last clock cycle. In this case we tested the inputs 1111, and made sure our AND gate worked properly, and surely enough it works. We can see

that F is high at the end of the simulation. We tested other functions and inputs as well, but we are just showing one waveform to keep things compact.

8 Work Division

Student	Task
Both	Pin-out Diagram.
Both	Explanation of how the chip works.
Both	Description of the major design decisions made.
Both	Inclusion and explanation of the test mode.
Silbak	VHDL LUT slice Module
Kasula	VHDL LUT slice Test Bench Module
Silbak	VHDL Top Level Module
Both	VHDL Top Level Test Bench Module
Silbak	LUT Slice Block Diagram
Kasula	LUT Slice Top Level Diagram

Table 3: Task Assignment

9 Magic Layouts

9.1 LUT Slice Layout

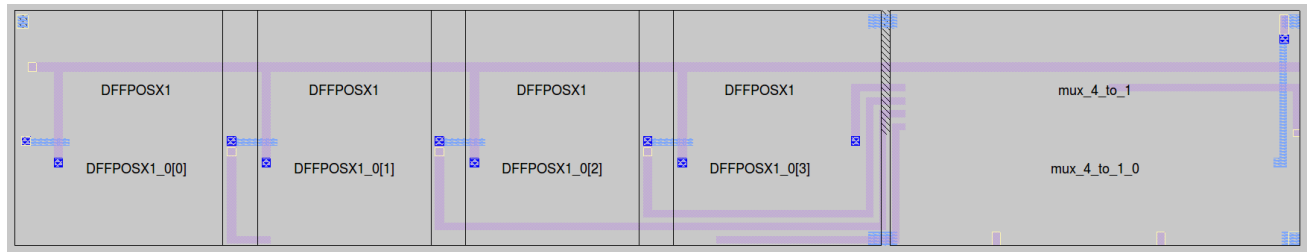


Figure 20: LUT Slice Magic Layout

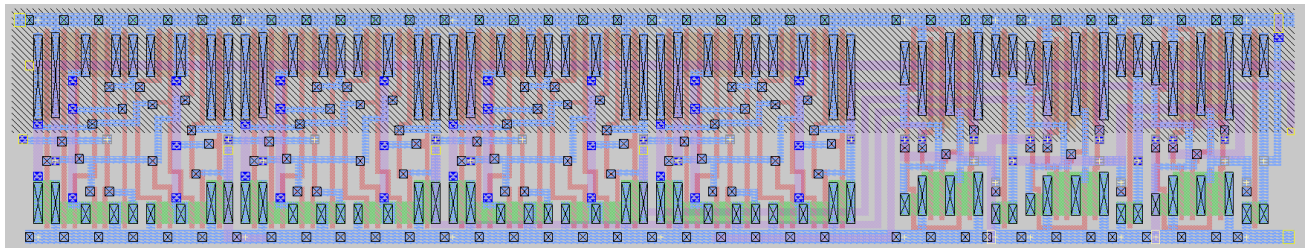


Figure 21: LUT Slice Internal Magic Layout

9.2 Shift Slice Layout



Figure 22: Shift Slice Magic Layout

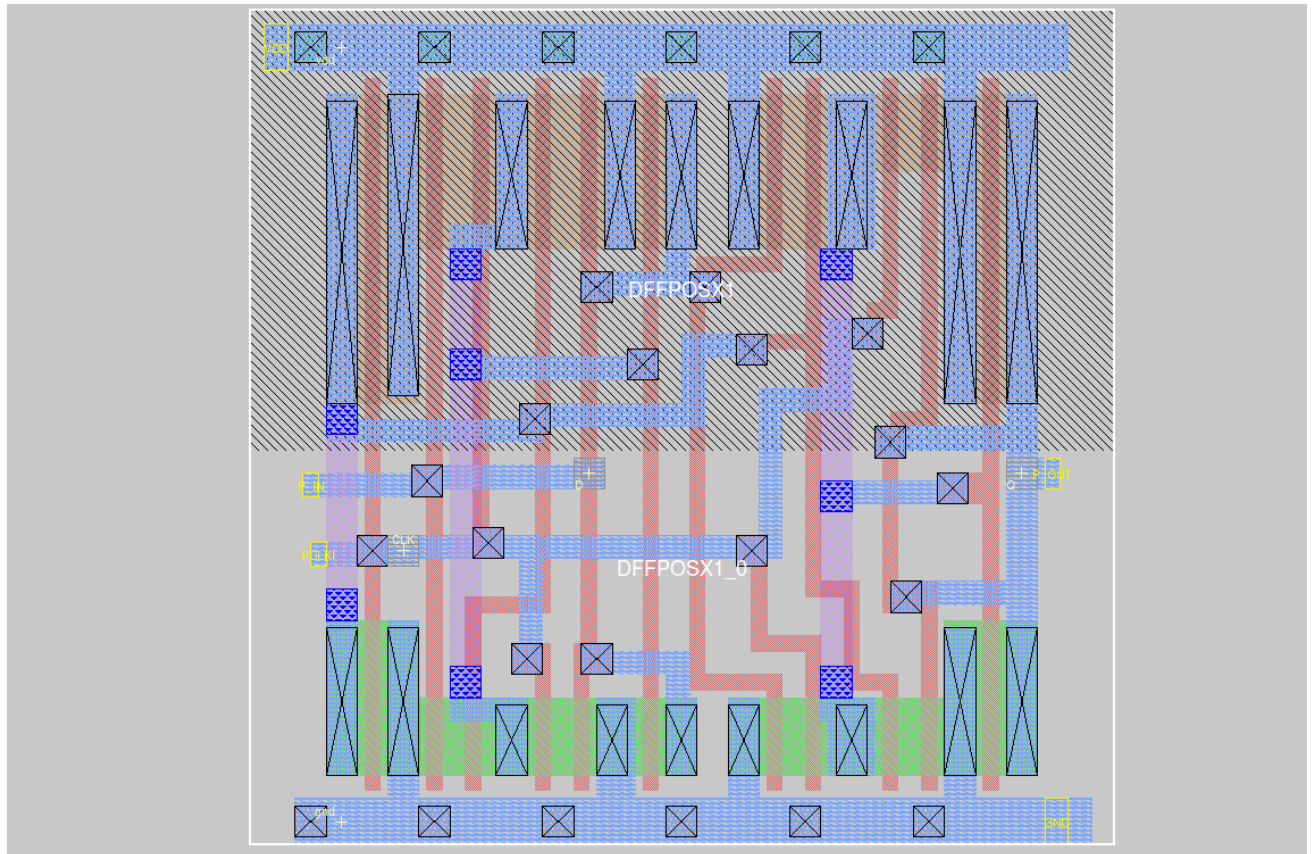


Figure 23: Shift Slice Internal Magic Layout

10 IRSIM Simulations

10.1 Bit Slice Simulations

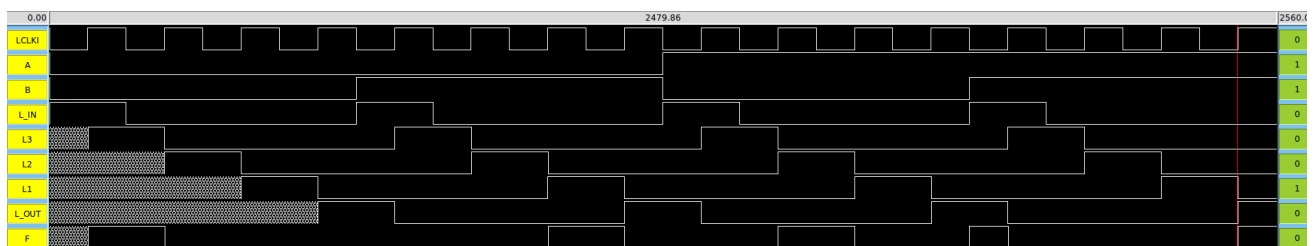


Figure 24: LUT Slice with AND gate 'programmed'

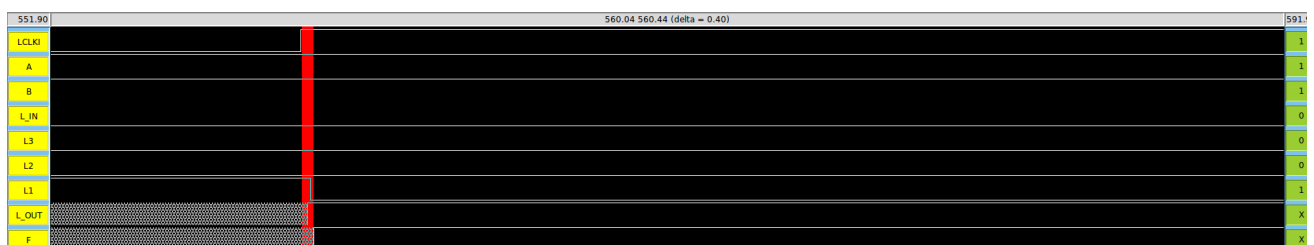


Figure 25: Rising Edge of F output of LUT Slice

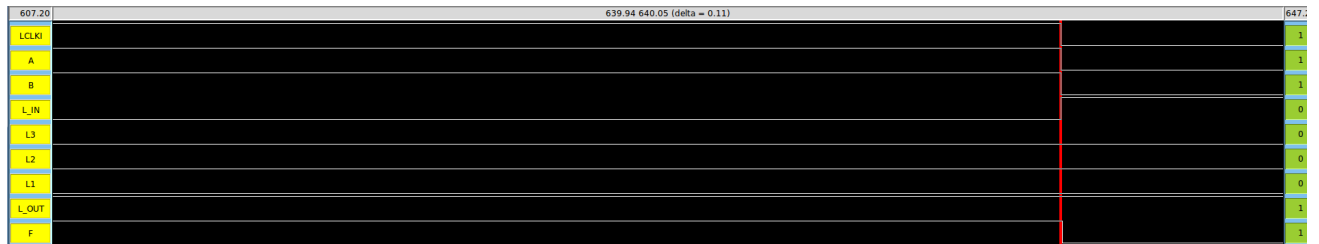


Figure 26: Falling Edge of F output of LUT Slice

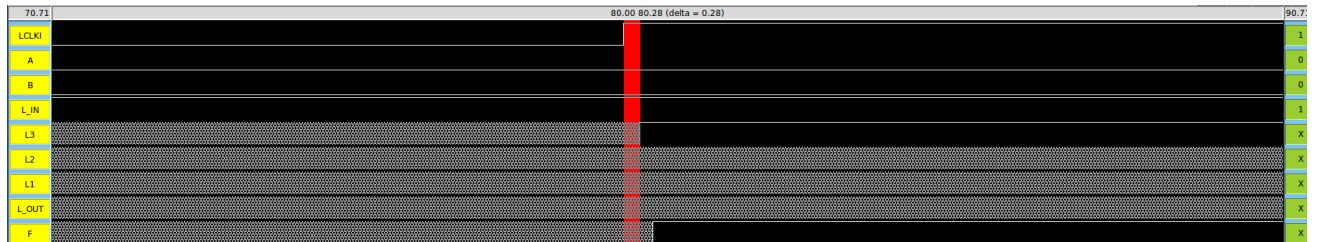


Figure 27: Rising Edge of L3 DFF of LUT Slice

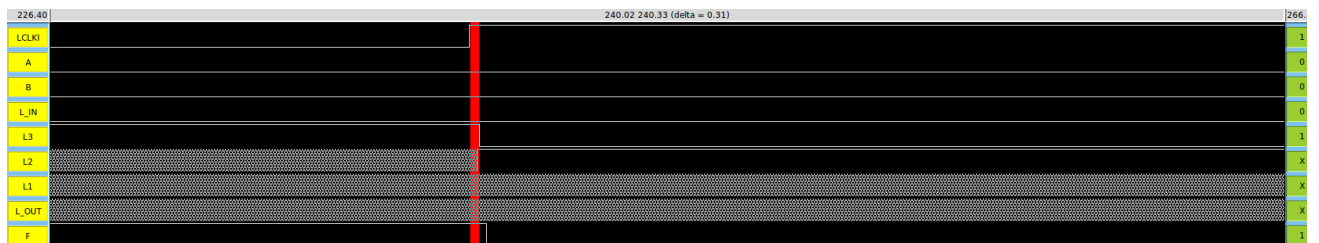


Figure 28: Falling Edge of L3 DFF of LUT Slice

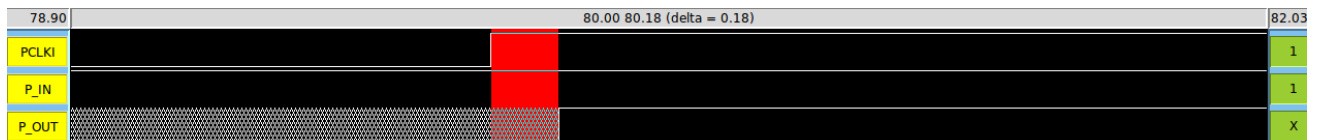


Figure 29: Rising Edge of DFF of Shift Slice

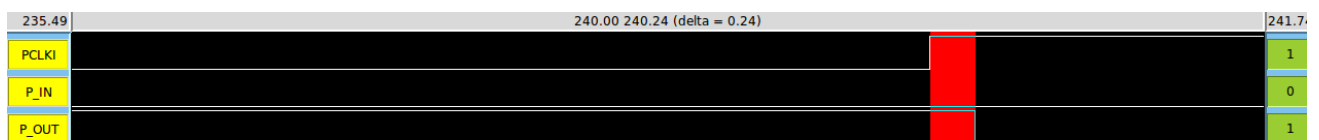


Figure 30: Falling Edge of DFF of Shift Slice

 


Figure 31: Waveform of DFF of Shift Slice

11 Gate Level Simulations

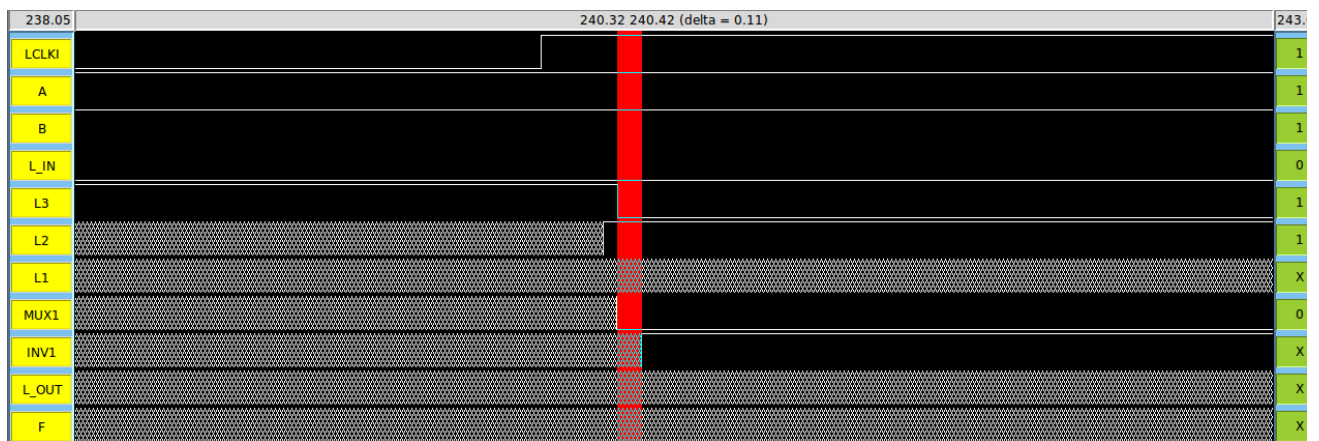


Figure 32: Rising Edge of Inverter

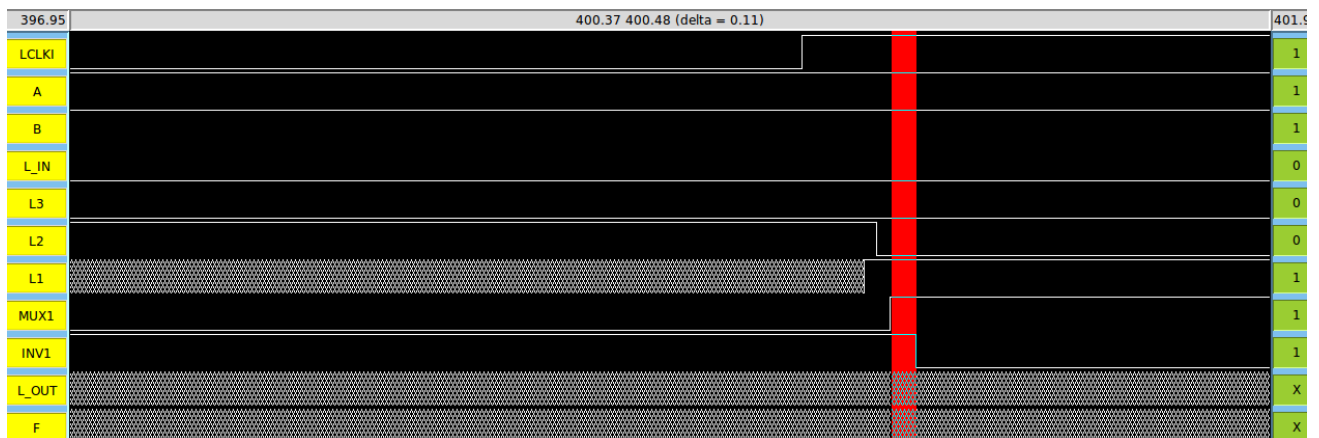


Figure 33: Falling Edge of Inverter

 


Figure 34: Waveform of LUT Slice (Includes nodes at each flip flop)

12 HSpice Simulations

12.1 Bit Slice Simulations

 


Figure 35: Hspice LUT Slice Waveform

 


Figure 36: Hspice Delay of Shift Register Slice

 


Figure 37: Hspice Shift Register Slice Waveform

12.2 Gate Level Simulations

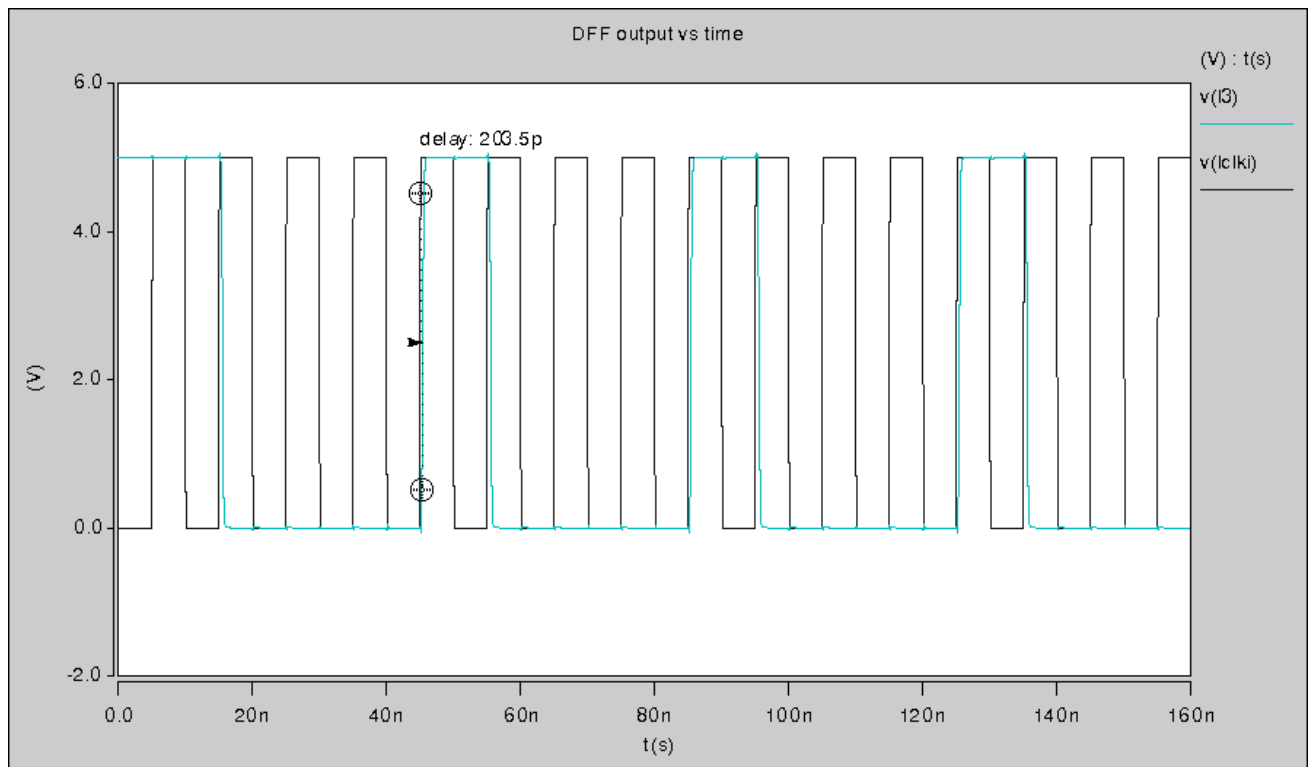


Figure 38: Hspice Delay of DFF

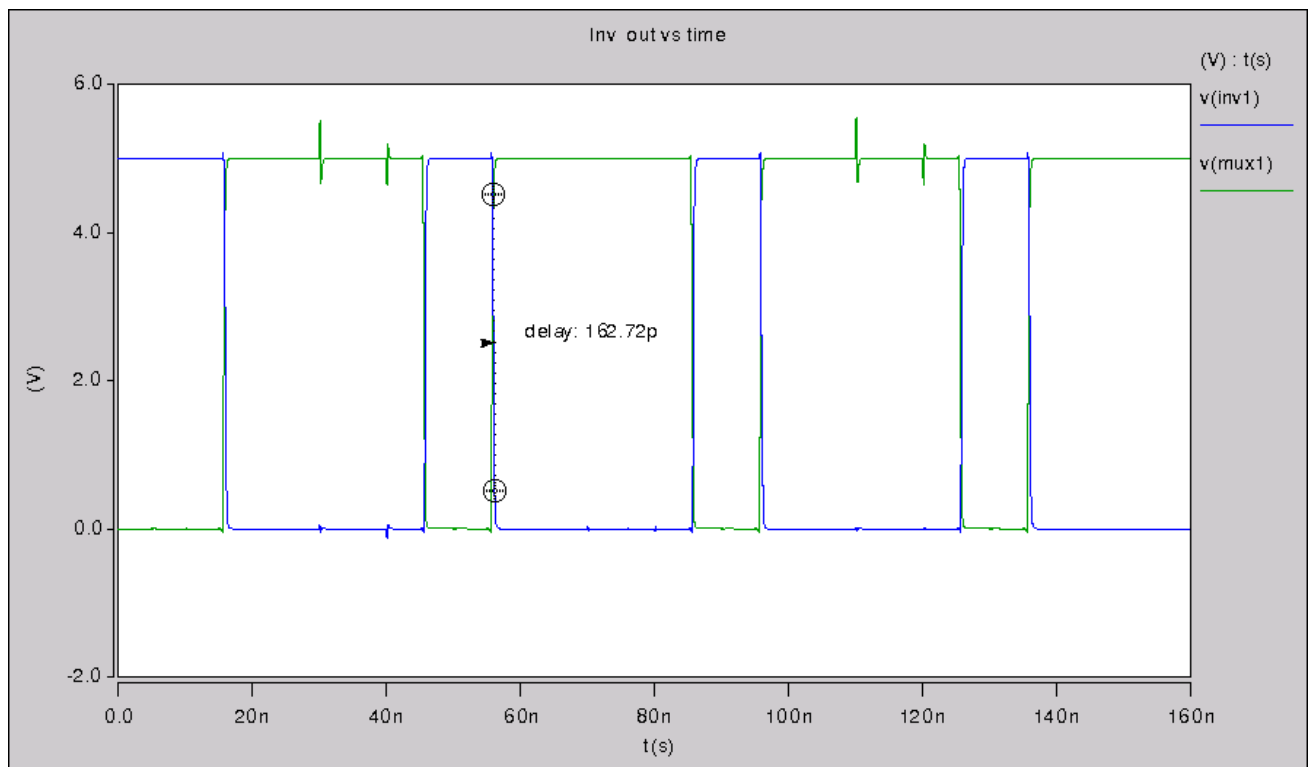


Figure 39: Hspice Delay of Inverter

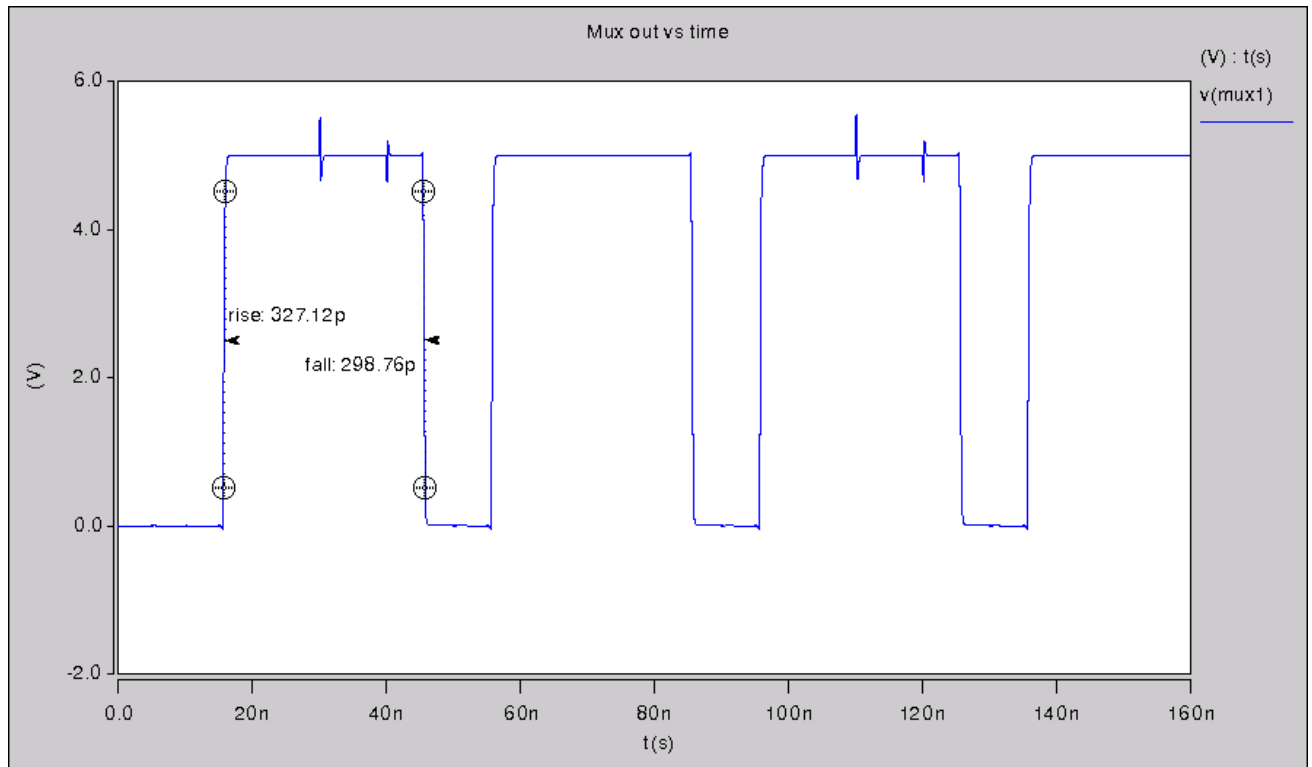


Figure 40: Hspice Delay of Mux

	IRSIM	VHDL	Hspice
Inverter	0.11 ns	0.159 ns	0.1627 ns
Mux	0.315 ns	0.312 ns	0.31214 ns
DFF	0.255 ns	0.198 ns	0.20305 ns

Table 4: Leaf Level Component Delay Times

13 VHDL Modules with Delay

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity top_del is
5      generic(
6          n          : integer := 2    — number of levels in tree
7      );
8      port(
9          p_clk : in std_logic;    — shift register clock
10         l_clk : in std_logic;    — lut shift register clock
11         p_in  : in std_logic;    — shift register input (P)
12         l_in  : in std_logic;    — lut shift register input
13         t_en  : in std_logic;    — test enable input
14         f_o   : out std_logic;   — final output of computation
15         q_o   : out std_logic;   — final lut shift register output
16     );
17 end top_del;
18
19 architecture rtl of top_del is
20
21     signal shift_clki    : std_logic := '0';
22     signal shift_clk    : std_logic := '0';
23     signal l_shf_ini     : std_logic := '0';
24     signal l_shf_in      : std_logic := '0';
25     signal p_out         : std_logic := '0';
26
27 begin
28
29     — test mux connects output of P into input of LUT and use same clock line
30     t_mux_1 : entity work.mux2x1_del port map(l_clk , p_clk , t_en , shift_clki);
31     t_mux_2 : entity work.mux2x1_del port map(l_in , p_out , t_en , l_shf_ini);
32
33     t_inv_1 : entity work.invx1_del port map(shift_clki , shift_clk);
34     t_inv_2 : entity work.invx1_del port map(l_shf_ini , l_shf_in);
35
36     lut_1 : entity work.lut_del
37         generic map(
38             n          => n
39         )
40         port map(
41             s_clk  => p_clk ,
42             l_clk  => shift_clk ,
43             s_in   => p_in ,
44             l_in   => l_shf_in ,
45             t_po   => p_out ,
46             f_o    => f_o ,
47             q_o    => q_o
48         );
49
50 end rtl;

```

Listing 8: Top Module Delay

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity lut_del is
5      generic(
6          n          : integer := 2    — number of levels in tree
7      );

```

```

8     port(
9         s_clk    : in std_logic;    — shift register clock
10        l_clk    : in std_logic;    — lut shift register clock
11        s_in     : in std_logic;    — shift register input (P)
12        l_in     : in std_logic;    — lut shift register input
13        t_po     : out std_logic;    — p_out for test mode
14        f_o      : out std_logic;    — final output of computation
15        q_o      : out std_logic    — final lut shift register output
16    );
17 end lut_del;
18
19 architecture rtl of lut_del is
20
21     — tree diagram for n = 3
22     — row 0 : A
23     — row 1 : BC
24     — row 2 : DEFG
25     — row 3 : shifter
26
27     — lut connection diagram
28     — l_in -> D -> E -> F -> G -> B -> C -> A
29
30     component dffposx1_del is
31     port(
32         clk : in std_logic;
33         d   : in std_logic;
34         q   : out std_logic
35     );
36 end component;
37
38     component lut_slice_del is
39     port(
40         clk_i : in std_logic;
41         d     : in std_logic;
42         a     : in std_logic;
43         b     : in std_logic;
44         q     : out std_logic;
45         f     : out std_logic
46     );
47 end component;
48
49     — carry_array(row, col)
50     type carry_array is array (0 to n, 0 to 2**n) of std_logic;
51     signal clk_c : carry_array;
52
53     — carries select outputs of one
54     — row to select inputs of next one
55     signal r_c : carry_array;
56
57     — carry output of each lut shift
58     — register
59     signal l_c : carry_array;
60
61     — input shift register carries
62     signal s_c : std_logic_vector(2**n downto 0) := (others => '0');
63
64     — input shift register clock carries
65     signal p_clk : std_logic_vector(2**n downto 0) := (others => '0');
66
67 begin
68
69     — generate the input shift register
70     shift_gen : for i in 0 to (2**n)-1 generate
71         ff_i : dffposx1_del

```

```

72     port map(
73         clk => s_clk ,
74         d   => s_c(i),
75         q   => s_c(i+1)
76     );
77 end generate shift_gen;
78
79 -- generate the tree
80 level_gen : for level in 0 to n-1 generate
81     lut_gen : for i in 0 to (2**level)-1 generate
82         lut_i : lut_slice_del
83             port map(
84                 clk_i => l_clk ,
85                 d     => l_c(level , i),
86                 q     => l_c(level , i+1),
87                 a     => r_c(level+1, i*2),
88                 b     => r_c(level+1, i*2+1),
89                 f     => r_c(level , i)
90             );
91         end generate;
92     end generate;
93
94 -- output the value of our function
95 q_o <= l_c(0, 1);
96 f_o <= r_c(0, 0);
97
98 -- connect each row of LUTs together
99 -- first slice in row i connects to
100 -- last slice in row i+1
101 lut_connect : for level in 0 to n-2 generate
102     l_c(level , 0) <= l_c(level+1, (2**level));
103 end generate;
104
105 -- connect input shift register to bottom row of slices
106 shift_connect : for i in 0 to (2**n)-1 generate
107     r_c(n, i) <= s_c(i+1);
108 end generate;
109
110 -- connect input to shift register
111 s_c(0) <= s_in;
112
113 -- connect input to first lut (bottom row)
114 l_c(n-1, 0) <= l_in;
115
116 -- use last slice of P shift register
117 -- feed it into LUT input for test mode
118 t_po <= s_c(2**n);
119
120 end rtl;

```

Listing 9: Look Up Table Module Delay

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity lut_slice_del is
6      port(
7          clk_i    : in std_logic;
8          d         : in std_logic;
9          a         : in std_logic;
10         b         : in std_logic;
11         q         : out std_logic;

```

```

12         f          : out std_logic
13     );
14 end lut_slice_del;
15
16 architecture rtl of lut_slice_del is
17
18     component dffposx1_del is
19         port(
20             clk : in  std_logic;
21             d   : in  std_logic;
22             q   : out std_logic
23         );
24     end component;
25
26     component invx1_del is
27         port(
28             a : in  std_logic;
29             x : out std_logic
30         );
31     end component;
32
33     component mux2x1_del is
34         port(
35             b : in  std_logic;
36             a : in  std_logic;
37             s : in  std_logic;
38             x : out std_logic
39         );
40     end component;
41
42     -- flip flop and mux outputs
43     signal ff_o      : std_logic_vector(4 downto 0) := (others => '0');
44     signal mux_o      : std_logic_vector(1 downto 0) := (others => '0');
45     signal mux_fo     : std_logic_vector(1 downto 0) := (others => '0');
46     signal f_muxo     : std_logic := '0';
47
48 begin
49
50     -- shifting in from LSB to MSB
51     shift_gen_lut : for i in 0 to 3 generate
52         ff_lut_i : dffposx1_del
53         port map(
54             clk => clk_i ,
55             d   => ff_o(i),
56             q   => ff_o(i+1)
57         );
58     end generate;
59
60     -- lut shift out is output from prev ff
61     q <= ff_o(4);
62     ff_o(0) <= d;
63
64     -- select first two outputs of LUT
65     -- on sel line A
66     mux1 : mux2x1_del port map(ff_o(1), ff_o(2), a, mux_o(0));
67     inv1 : invx1_del  port map(mux_o(0), mux_fo(0));
68
69     -- select last two outputs of LUT
70     -- on sel line A
71     mux2 : mux2x1_del port map(ff_o(3), ff_o(4), a, mux_o(1));
72     inv2 : invx1_del  port map(mux_o(1), mux_fo(1));
73
74     -- select the outputs from
75     -- each mux on sel line B

```

```

76     mux3 : mux2x1_del port map(mux_fo(0), mux_fo(1), b, f_muxo);
77
78     -- invert mux due to func of mux: y = !(S?(A:B))
79     inv3 : invx1_del port map(f_muxo, f);
80
81 end rtl;

```

Listing 10: Look Up Table Slice Module Delay

13.1 VHDL Test Bench Modules with Delay

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use std.textio.all;
4  use work.txt_util.all;
5
6  entity top_test_del_tb is
7  end top_test_del_tb;
8
9  architecture behavior of top_test_del_tb is
10
11     constant n : integer := 5;
12
13     component top_del
14         generic(
15             n      : integer := 3    -- number of levels in tree
16         );
17         port(
18             p_clk : in std_logic;    -- p shift register clock
19             l_clk : in std_logic;    -- lut shift register clock
20             p_in  : in std_logic;    -- shift register input (P)
21             l_in  : in std_logic;    -- lut shift register input
22             t_en  : in std_logic;    -- test enable input
23             f_o   : out std_logic;   -- final output of computation
24             q_o   : out std_logic;   -- lut shift register output
25         );
26     end component;
27
28     signal p_clk : std_logic := '0';
29     signal l_clk : std_logic := '0';
30     signal p     : std_logic := '0';
31     signal l_in  : std_logic := '0';
32     signal f_o   : std_logic;
33     signal q_o   : std_logic;
34     signal t_en  : std_logic := '0';
35
36 begin
37
38     dut : top_del
39         generic map(
40             n      => n
41         )
42         port map(
43             p_clk => p_clk,
44             l_clk => l_clk,
45             p_in  => p,
46             l_in  => l_in,
47             t_en  => t_en,
48             f_o   => f_o,
49             q_o   => q_o
50         );
51

```

```

52     process
53
54         procedure clk is begin
55             p_clk <= '1';
56             wait for 10 ns;
57             p_clk <= '0';
58             wait for 10 ns;
59         end procedure clk;
60
61     begin
62
63         wait for 10 ns;
64         -- enable test mode
65         t_en <= '1';
66
67         -- clock in p data
68         p <= '1';
69         wait for 10 ns;
70         clk;
71
72         -- clock in p data
73         p <= '0';
74         wait for 10 ns;
75         clk;
76
77         -- # of FF's per LUT: 4
78         -- # of LUT FF's      : (((2**n)-1)*4)
79         -- # of P FF's       : 2**n
80         -- subtract 2 since we just loaded in two inputs
81         for i in 0 to (((2**n)-1)*4)+2**n-2-1 loop
82             clk;
83         end loop;
84
85         wait;
86
87     end process;
88
89 end behavior;

```

Listing 11: Test Mode Enabled Test Bench

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use std.textio.all;
4  use work.txt_util.all;
5
6  entity top_del_tb is
7      generic(
8          --stim_file : string := "test_tree.sim"
9          --stim_file : string := "two_tree.sim"
10         stim_file : string := "top_32.sim"
11     );
12 end top_del_tb;
13
14 architecture behavior of top_del_tb is
15
16     constant n : integer := 5;
17
18     signal p_clk : std_logic := '0';
19     signal l_clk : std_logic := '0';
20     signal p     : std_logic := '0';
21     signal l_in  : std_logic := '0';
22     signal f_o   : std_logic;

```

```

23  signal q_o    : std_logic;
24  signal t_en   : std_logic := '0';
25
26  signal p_in_vector : std_logic_vector((2**n)-1 downto 0);
27  signal lut_vector  : std_logic_vector((((2**n)-1)*4)-1 downto 0);
28
29  file stimulus : TEXT open read_mode is stim_file;
30
31  component top_del
32    generic(
33      n      : integer := 3    -- number of levels in tree
34    );
35    port(
36      p_clk : in std_logic;    -- p shift register clock
37      l_clk : in std_logic;    -- lut shift register clock
38      p_in  : in std_logic;    -- shift register input (P)
39      l_in  : in std_logic;    -- lut shift register input
40      t_en  : in std_logic;    -- test enable input
41      f_o   : out std_logic;   -- final output of computation
42      q_o   : out std_logic    -- lut shift register output
43    );
44  end component;
45
46  begin
47
48    dut : top_del
49      generic map(
50        n      => n
51      )
52      port map(
53        p_clk => p_clk ,
54        l_clk => l_clk ,
55        p_in  => p ,
56        l_in  => l_in ,
57        t_en  => t_en ,
58        f_o   => f_o ,
59        q_o   => q_o
60      );
61
62    process
63
64      procedure clk_p_in is begin
65        p_clk <= '1';
66        wait for 10 ns;
67        p_clk <= '0';
68        wait for 10 ns;
69      end procedure clk_p_in;
70
71      procedure clk_lut_in is begin
72        l_clk <= '1';
73        wait for 10 ns;
74        l_clk <= '0';
75        wait for 10 ns;
76      end procedure clk_lut_in;
77
78      variable l : line;
79      variable p_in_str : string(1 to 2**n);
80      variable l_shf_str : string(1 to ((2**n)-1)*4);
81
82    begin
83
84      while not endfile(stimulus) loop
85
86        -- load stimulus for this test

```

```

87         readline(stimulus, l); read(l, p_in_str);
88         p_in_vector <= to_std_logic_vector(p_in_str);
89
90         readline(stimulus, l); read(l, l_shf_str);
91         lut_vector <= to_std_logic_vector(l_shf_str);
92
93         wait for 50 ns;
94
95         — clock in the P input
96         for i in 0 to (2**n)-1 loop
97             p <= p_in_vector(i);
98             wait for 10 ns;
99             clk_p_in;
100         end loop;
101
102         — clock in the "program" (lut functions)
103         for i in 0 to (((2**n)-1)*4)-1 loop
104             l_in <= lut_vector(i);
105             wait for 10 ns;
106             clk_lut_in;
107         end loop;
108
109     end loop;
110
111     report "Test Complete" severity note;
112     wait;
113
114 end process;
115
116 end behavior;

```

Listing 12: Top Module Test Bench

13.2 VHDL Gate Modules with Delay

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity dffposx1_del is
5      generic(
6          delay : time := 203.5 ps
7      );
8      port(
9          clk : in std_logic;
10         d   : in std_logic;
11         q   : out std_logic
12     );
13 end dffposx1_del;
14
15 architecture rtl of dffposx1_del is begin
16     process(clk) begin
17         if rising_edge(clk) then
18             q <= d after delay;
19         end if;
20     end process;
21 end rtl;

```

Listing 13: DFF Module Delay

```

1  library ieee;
2  use ieee.std_logic_1164.all;

```



```

3
4  entity invx1_del is
5      generic(
6          delay : time := 162.7 ps
7      );
8      port(
9          a : in std_logic;
10         x : out std_logic
11     );
12 end invx1_del;
13
14 architecture rtl of invx1_del is begin
15     x <= not a after delay;
16 end rtl;

```

Listing 14: Inverter Module Delay

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity mux2x1_del is
5      generic(
6          delay : time := 315 ps
7      );
8      port(
9          b : in std_logic;
10         a : in std_logic;
11         s : in std_logic;
12         x : out std_logic
13     );
14 end mux2x1_del;
15
16 architecture rtl of mux2x1_del is begin
17
18     x <= not(b) after delay when (s = '0') else
19         not(a) after delay when (s = '1');
20
21 end rtl;

```

Listing 15: Inverter Module Delay

14 VHDL Modules Delay Waveforms

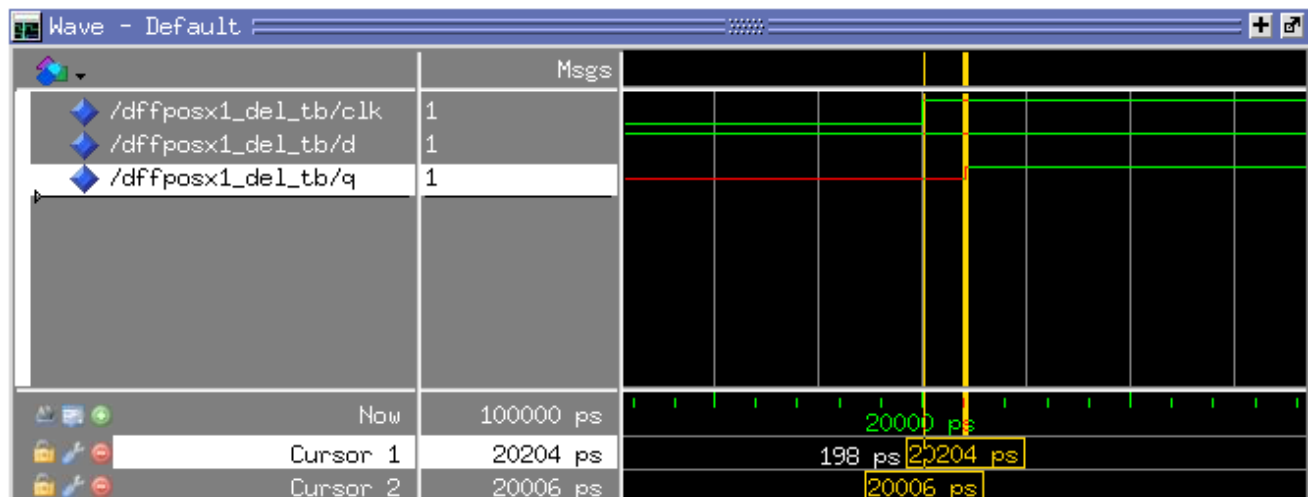


Figure 41: Delay Waveform of DFF

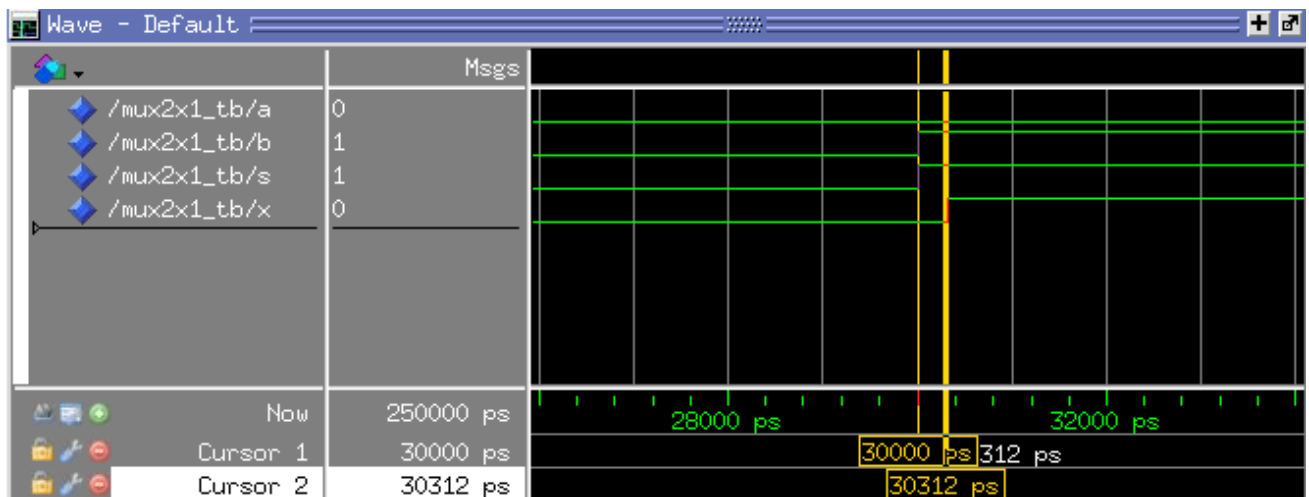


Figure 42: Delay Waveform of MUX

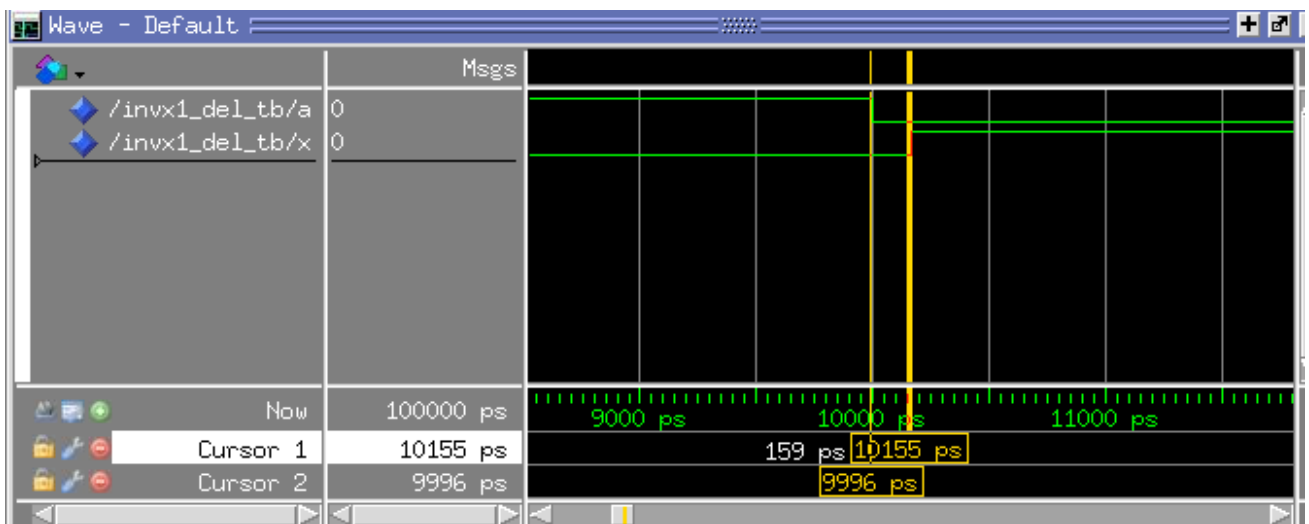


Figure 43: Delay Waveform of Inverter

In table 4, we compare the delay results for each leaf level gate among the three design simulations. Please look at the figures listed above. We can see that these compare very well with each other. Also, note that in order to calculate the total delay time of the LUT slice, we must add up the delay values found from four D flip flops, three muxes, and three inverters. After adding them up, our LUT slice circuit gets a delay time of approximately ~2 ns. Also, note that in order to get maximum clock rate, we just take the worst case delay of our circuit, and use this as a maximum clock rate. The table and figures above give us a worst case delay which is above the 50Mhz desirable signal.

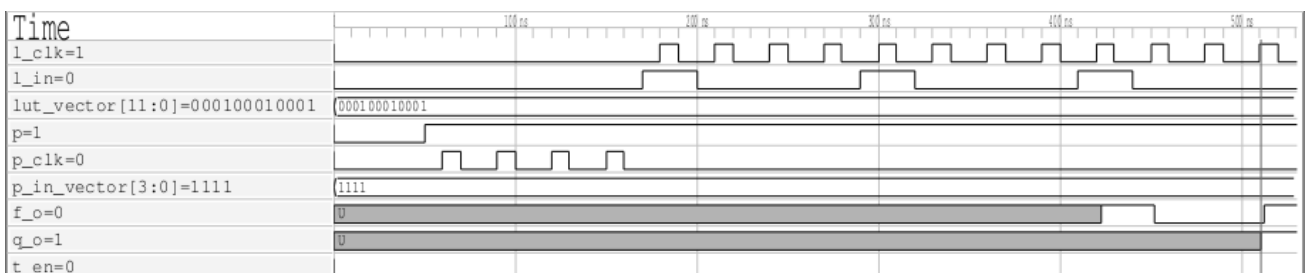


Figure 44: Top Level Delay Waveform

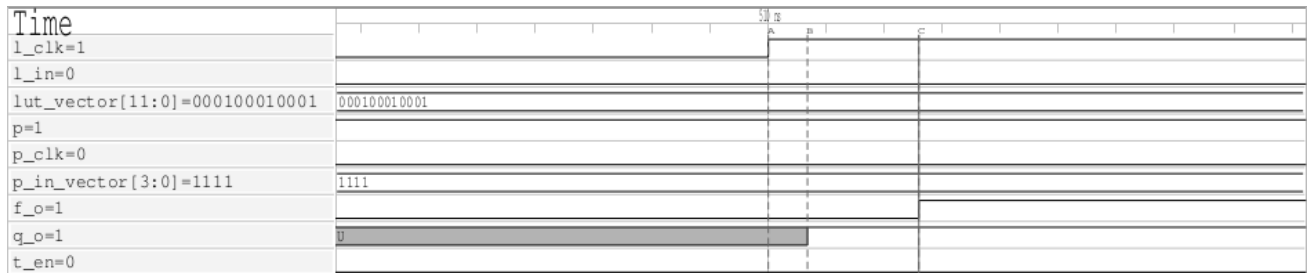


Figure 45: Top Level Delay Waveform Zoomed In

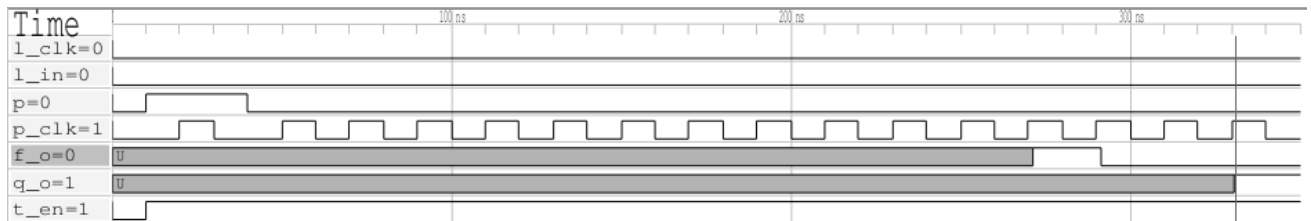


Figure 46: Top Level Test Mode Enabled Delay Waveform



Figure 47: Top Level Test Mode Enabled Delay Waveform Zoomed In

As we can see here, the circuit still functions correctly given the delay times extracted from the simulations we have exhaustively gone through. This compares well with the previous simulation because as I have mentioned the functionality of the circuit still works properly. Also, we went ahead and measured the delay time for both the final Q and F output. In the above figure, the total delay time from A to B (Q output) was found to be 0.690 ns and from A to C (F output) was found to be ~ 2.6 ns (worst case delay). This tells us that maximum clock speed achieved can be $1/2.6\text{ns} \sim 384.6153846$ MHz.

	IRSIM	VHDL	Hspice
LUT Slice	2.295 ns	2.6 ns	2.2375 ns
P Slice	0.255 ns	0.198 ns	0.20305 ns

Table 5: Bit Slice Worst Case Delay Times

15 Floor Plan

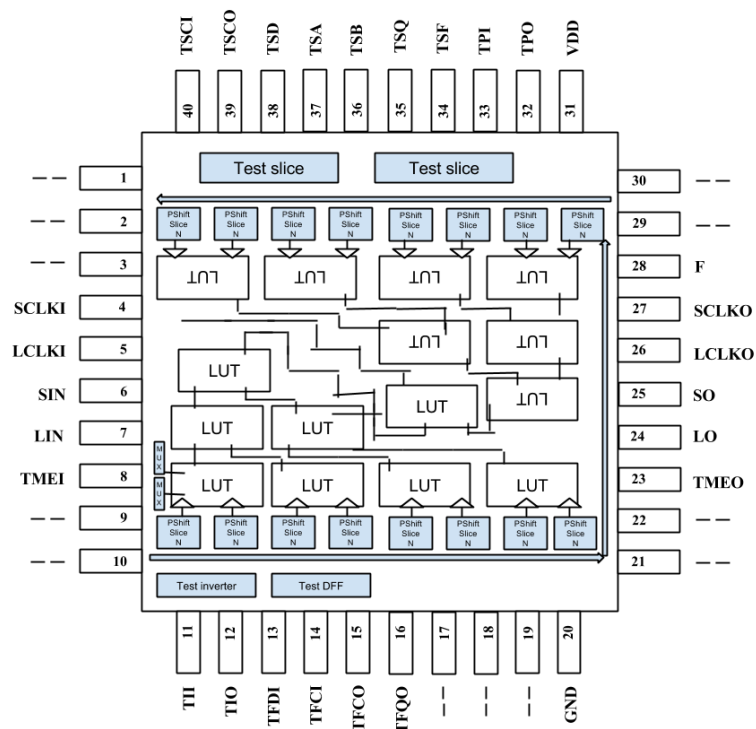


Figure 48: 32 Bit Floor Plan Design

This is the initial floor plan we designed. Note that in this design, we see a maximum of 16 inputs, this was just to show how it is to be designed in magic. In fact our actual design will consist of a maximum 32 inputs. Therefore, our design will have a total of 156 ($32 + 31 \cdot 4$) D flip flops.

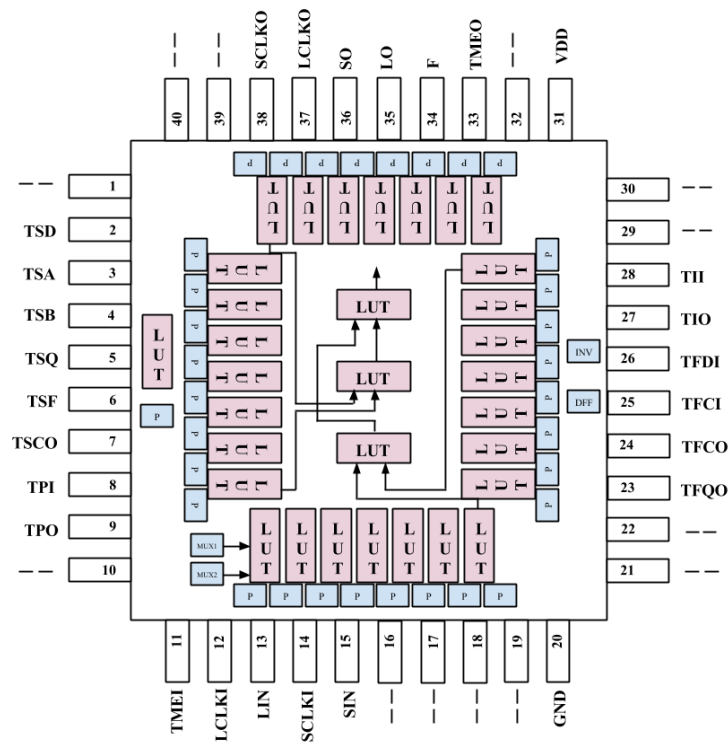


Figure 49: 64 Bit Floor Plan Design

This is the initial floor plan we designed for the 64 bit layout. Note that in this design, we see a maximum of 32 inputs, this was just to show how it is to be designed in magic. In fact our actual design will consist of a maximum 64 inputs. Therefore, our design will have a total of 316 ($64 + 63 \cdot 4$) D flip flops. Not only does our design officially maximize N , but maximizes the total area used as well.

16 Major Design Decisions

We had to think of how to design our layout before we could come up with a floor plan. Since we have a binary tree, it was quite difficult to come up with an efficient way to utilize the whole area available given to us. At first, we thought we could fold the LUTs against each corner of the frame, but in doing so, led to a lot of wasted space in the middle. Therefore, we decided to go back and redesign the top level diagram of our circuit since constructing the layout in a binary tree manner would be very inefficient. The new top level design can be seen in Figure 4. The slices themselves are not changed, only the way these slices are arranged (laid out) have changed.

17 Work Division

Student	Task
Both	Modified Pin-out Diagram
Both	Magic Layout
Both	HSPICE
Both	IRSIM
Both	VHDL
Both	Floor Plan

Table 6: Task Assignment

18 Chip Level Layout

 


Figure 50: 32 Bit Layout - Magic

19 Users Guide

 


Figure 51: Cycle Timing Diagram for Normal Mode

In normal mode, the user will need to leave the TMEI signal low. The user will then need to give data inputs to both PI and LI. Since, LI has 4 times the number of bits that P has, LCLK should then be triggered for 4 times longer than PCLK. The final computation is shown to be on the very last clock cycle. Also, it does not matter whether the P input or LUT inputs are loaded in first, the functionality of the circuit will still remain working properly. Note to the user, in this timing diagram, we are showing that P input is loaded in first.

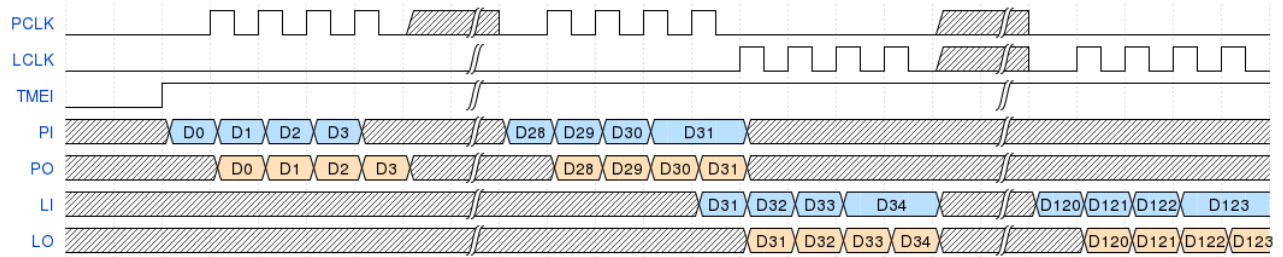


Figure 52: Cycle Timing Diagram for Test Mode Enable

In test mode, we are connecting all the D-Flip Flops together to make sure all the flip flops are shifting properly. This scheme is known as a scan chain. Here we can see that when TMEI is high, we are in test mode. The output of the last clock signal and data output of P will be connected to the input of the LCLK and LI, respectively. Since the architecture contains 32 bits for the P input and 124 (31×4) bits for the LUT, we will have to shift in a vector of 156 bits ($124 + 32$) in order to see the output of the scan chain. Only then can the user monitor the output to verify that all the shift registers are working as intended. Note that F (the final computation) is not shown in this timing diagram, because the user is not concerned with the functionality of the LUTs in this mode—only monitoring the shift registers.

The user will need to set TMEI high, then he/she will have to give the data inputs to PI and make sure to have a total of 156 clock cycles for PCLK, the rest is taken care of by the hardware (the user will not have to give any inputs to the LUT).

20 Test Strategy

We have a few methods for testing to ensure that the chip is working correctly. The first method we use for testing purposes is to connect all the D-Flip Flops together to create the initial scan chain. This will allow the user to make sure all of the shift registers are working properly. Another method, is to have individual bit slice designs completely independent of the circuit itself. Therefore, we have the Look Up Table Slice and the P-shift register slice completely independent of the circuit. The third method consists of having separate standard slices, both an inverter and a D-Flip Flop completely independent of the circuit as well. The final method consists of monitoring certain signals within each cell. Other testing strategies include looking at the clock output signals and making sure that the signal follows the input clock signals. If the user ensures these signals are not lagging, then it's safe to conclude that the signal strength provided by the buffers are sufficient enough to overcome the capacitance.

In the first method, the user will only need to pull the TMEI pin high.

In the second method, the user will need to feed the individual bit slice inputs as noted:

LUT slice:

TSCI (test slice clock input) is the input to the clock line.

TSD (test slice D input) is the input to the LUT, the user will shift in the combinational function he/she desires to test.

TSA and TSB (test slice A and B) are inputs and act as the address lines into the LUT, the user should feed these inputs after “programming” the LUT.

TSQ is the output of the LUT, the user can probe this pin to make sure everything that was shifted in is correct. F is the output of the final computation the LUT slice performs. The user can probe this pin to monitor that the final computation is working as intended.

TSCO (test slice clock output) is the output to the clock line.

P Shift register Slice:

TSCI (test slice clock input) is the input to the clock line.

TSPI (test slice p input) is the input to the signal P.

TSPO (test slice p output) is the output signal of P.

The third method consists of two separate standard cells, the inverter and the DFF:

Inverter:

TII (test inverter input) is the input to the inverter, the user will give this pin any value.

TIO (test inverter output) is the output to the inverter, the user will probe this pin to monitor the output.

D-Flip Flop:

TFCI (test flip flop clock input) is the input to the test clock line, the user will give this pin the clock signal.

TFDI (test flip flop D input) is the input to the D-Flip Flop, the user will give this pin an input value to be monitored.

TFQO (test flip flop Q output) is the output of the D-Flip Flop, the user will use this pin to monitor the output.

TFCO (test flip flop clock output) is the output of the clock line.

For the last and final method, we have certain pins used to monitor certain various areas within the circuit. The user should use the Pin description to see each output pin needed to test to ensure the functionality of the circuit is performing correctly.

21 Description of Chip Architecture

The PBCTKS architecture uses a 32-bit wide P register and a 124-bit wide LUT register for programming mode. This allows the user to program up to 2^{32} different combinations for given inputs and $2^{(124/4)}$ different combinations to program the functionality of the chip. This chip consists of ~31 I/O pins which include test pins for testing purposes, and includes a pin to set the chip in normal or testing mode.

22 Major Design Decisions

We layed everything out in magic, and noticed that we would only be using about 60% of chip area. This was just unacceptable, so we needed to come up with a different layout design where we would be able utilize more of the chip area. We decided to design how we needed to rearrange the slices in a more compact fashion. In Figure 49, we can see the method of the layout that would have been used in Magic.

Unfortunately, we were very constrained with time, and connecting the VDD and GND lines became exponentially complicated that we had to stop and revert back to the 32 bit design. The incomplete 64 bit design can be shown below.

 


Figure 53: 64 Bit Layout in Magic

Here we can see that we maximized not only N, but the total area that was given to us. But as I have mentioned previously, due to wiring complexity and timing constraints, we were not able to complete this on time and had to revert back to the original 32 bit design.

DFFPOSX1	Capacitance (pF)
CLK	~0.05
D	~0.0157

Table 7: Capacitance Values for D-Flip-Flop

BUFFX4	Capacitance (pF)	Cap Output Drive Strength (pF)
A	~0.0322	1.85
Y	~0.0322	

Table 8: Capacitance Value and Output Drive Strength for Buffer

Since the clock signal was global and driving all of the slices, we needed to accommodate for the capacitance. In the table above we can see that the capacitance of the D-Flip Flop was found to be 0.05pF. Therefore, we

knew that this capacitance would add up over all of the bit slices, so we needed to make sure to add buffers when needed. The table above shows the output drive strength for the given buffer. We then used this to calculate the maximum buffers that could be used: $1.85\text{pF} / 0.05\text{pF} \sim 37$. Therefore, we ended up just putting a buffer every 32 DFFs (leaving 5 for error).

23 IRSIM Simulations

 


Figure 54: Top Delay Normal Mode

We can see the worst case delay time found in IRSIM shown in the above picture. This is very consistent with what we have seen in our VHDL design.

 


Figure 55: Test LUT Slice

We can see that the independent LUT slice works correctly.

 


Figure 56: Test P Shift Register Slice

We can see that the independent P Shift Register slice works correctly.

 


Figure 57: Test DFF Slice

We can see that the independent DFF slice works correctly.

 


Figure 58: Inverter

We can see that the independent Inverter works correctly.

24 VHDL Simulations



Figure 59: Top 32-bit Normal Mode



Figure 60: Top 32-bit Test Mode

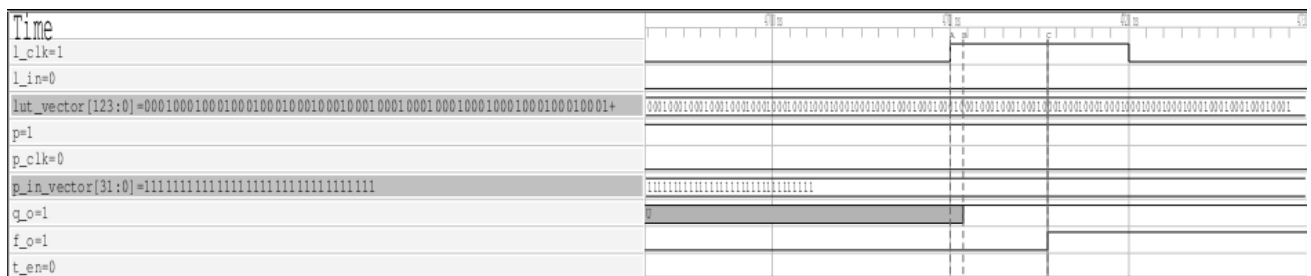


Figure 61: Top Delay 32-bit Normal Mode

 


Figure 62: Top Delay 32-bit Test Mode

	VHDL	IRSIM
F	5.470 ns	6.32 ns

Table 9: Total Delay Times for Normal Mode between VHDL and IRSIM

F is the final output computation for the Look Up Table (this was our worst case delay). We can see here that the times are fairly close to one another. Note this is the total delay, but keep in mind that the delay per slice for worst case delay was found to be 2.6ns. So our Maximum clock frequency is found to be $1/2.6\text{ns}$, approximately 385 MHz.

25 Simulation Strategy

It was much easier to use Python to write to the cmd file, and then check the output log file if anything failed. It would be too difficult to give a 124 bit vector manually, so we used Python to feed the signals for both in VHDL and IRSIM. Also, since we want to make sure things works as intended, the best method was to just shift in all 1's for all the DFF, and monitor the outputs accordingly. This gave us an idea if something was being shorted out

or something was not shifting out properly. Then we monitored each node for debugging purposes to ensure that each bit was being shifted out from one flip flop to the next. A figure below shows the method used.

 


Figure 63: Debug Mode in IRSIM

26 Work Division

Student	Task
Both	Modified Pin-out Diagram
Both	Magic Layout
Both	IRSIM
Both	VHDL
Both	Modified Floor Plan

Table 10: Task Assignment